
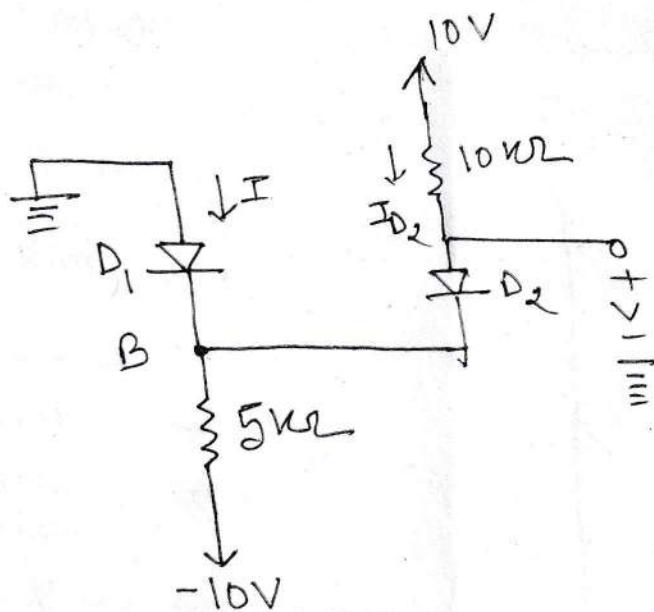


4.2(a)

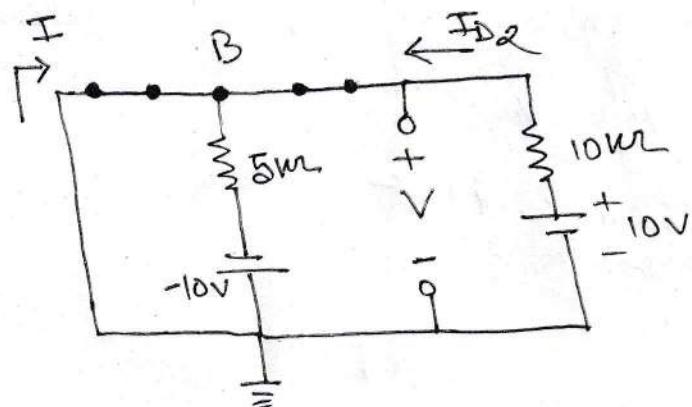

Sol<sup>m</sup>.

Let assume the diode  $D_1$  &  $D_2$  are conducting.  
We can redraw the circuit as,



Therefore,  $V = 0\text{V}$  ~~at node O~~ and  $I_{D_2} = \frac{10-V}{10} = 1\text{mA}$

Applying nodal analysis at node  $B$ , we get,

$$I + I_{D_2} = \frac{V - (-10)}{5}$$

$$\Rightarrow I + \frac{10-V}{10} = \frac{V+10}{5}$$

$$\Rightarrow I + 1 = 2$$

$$\Rightarrow I = 2 - 1$$

$$\therefore I = 1\text{mA} \quad (\text{Ans})$$

\* In the forward region, the i-v relationship is closely approximated by,

$$i = I_s (e^{v/v_T} - 1) \quad (\text{i})$$

where,  $i$  = diode current

$I_s$  = saturation current

$$v_T = \text{thermal voltage} = \frac{kT}{q} \approx 25.3 \text{ mV}$$

at room temperature ( $20^\circ\text{C}$ )

As  $i \gg I_s$ , eqn (i) can be written as

$$i \approx I_s e^{v/v_T} \quad (\text{ii})$$

Now, for the diode voltage  $v_1$ , the diode current  $I_1$ ,

$$I_1 = I_s e^{v_1/v_T} \quad (\text{iii})$$

Similarly, for a voltage  $v_2$ , the diode current  $I_2$

$$I_2 = I_s e^{v_2/v_T} \quad (\text{iv})$$

$$\text{Now, eqn}\{(iv) \div (iii)\} \Rightarrow \frac{I_2}{I_1} = e^{(v_2-v_1)/v_T}$$

$$\Rightarrow v_2 - v_1 = v_T \ln \frac{I_2}{I_1}$$

~~$$\text{or } v_2 - v_1 = 2.3 \log \frac{I_2}{I_1}$$~~

$$\text{or, } v_2 - v_1 = 2.3 v_T \log \frac{I_2}{I_1}$$

### Example 4.3 (Ch-4, SM)

A silicon diode said to be a 1 mA device displays a forward voltage of 0.7 V at a current of 1 mA. Evaluate the junction scaling constant  $I_S$ . What scaling constants would apply for a 1-A diode of the same manufacture that conducts 1 A at 0.7 V?

Solution: we know,  $i = I_S e^{v/VT}$

$$\Rightarrow 10^{-3} = I_S \times e^{\frac{0.7}{25 \times 10^{-3}}}$$
$$\Rightarrow I_S = 6.9 \times 10^{-16} \text{ A.} \quad (\text{Ans.})$$

The diode conducting 1 A at 0.7 V corresponds to one-thousand 1 mA diodes in parallel with a total junction area 1000 times greater. Therefore,  $I_S$  will be 1000 times greater.

$$\therefore I_S = 1000 \times 6.9 \times 10^{-16} = 6.9 \times 10^{-13} \text{ A.} \quad (\text{Ans.})$$

\*\*) Practise exercises 4.6 & 4.7 [Ch-4, SM, P-188]

### Example 4.4 (ch-4, sm, p-192)


Determine the current  $I_D$  and the diode voltage  $V_D$  for the circuit with  $V_{DD} = 5V$  and  $R = 1k\Omega$ .

Assume that the diode has a current of 1 mA at a voltage of 0.7 V.

Solution: If  $V_D = 0.7V$  then,

$$I_D = \frac{V_{DD} - V_D}{R}$$
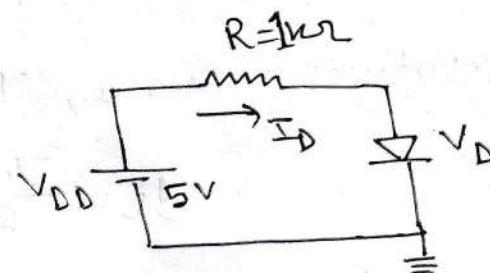
$$= \frac{5 - 0.7}{1} = 4.3 \text{ mA.}$$



We know,

$$V_{D2} - V_{D1} = 2.3 V_T \log \frac{I_{D2}}{I_{D1}}$$

$$\Rightarrow V_{D2} - 0.7 = 2.3 \times (25 \times 10^{-3}) \times \log \frac{4.3}{1}$$

$$\Rightarrow V_{D2} = 0.738 \text{ V}$$

For  $V_D = 0.738 \text{ V}$ ,

$$\therefore I_D = \frac{V_{DD} - V_D}{R} = \frac{5 - 0.738}{1} = 4.262 \text{ mA}$$

NOW,  $V_{D3} - V_{D2} = 2.3 V_T \log \frac{I_{D3}}{I_{D2}}$

$$\Rightarrow V_{D3} - 0.738 = 2.3 \times (25 \times 10^{-3}) \log \frac{4.262}{4.3}$$

$$\therefore V_{D3} = 0.738 \text{ V.}$$

^further

Therefore, no iterations are necessary.

$$\therefore I_D = 4.262 \text{ mA and } V_D = 0.738 \text{ V. (Ans.)}$$

**Clonatril®**  
clonazepam



\*\*) Practise Ex 4.10 [ch-4, sm, p-194].

Exercise D4.11 [Ch-4, SM, p-194]

Design the circuit in Fig. to provide an output voltage of 2.4 V. Assume that the diodes available have 0.7 V drop at 1 mA.

Solution: Here,  $V_o = 2.4 \text{ V}$

$$\therefore V_D = \frac{V_o}{3} = 0.8 \text{ V}$$

We know,

$$V_{D_2} - V_{D_1} = 2.3 V_T \log \frac{I_{D_2}}{I_{D_1}}$$

$$\Rightarrow 0.8 - 0.7 = 2.3 \times (25 \times 10^{-3}) \times \log \frac{I_{D_2}}{1}$$

$$\therefore I_{D_2} = 54.84 \text{ mA.}$$

$$\therefore R = \frac{V_{DD} - V_o}{I_{D_2}} = \frac{10 - 2.4}{54.84}$$

$$= 0.139 \text{ k}\Omega$$

$$= 139 \Omega$$


(Ans.)

\*\*) Practice


EX: 4.9, 4.23, 4.28, 4.35, 4.58 [Ch-4, SM, at the end of the chapter].

\*\*) Practice

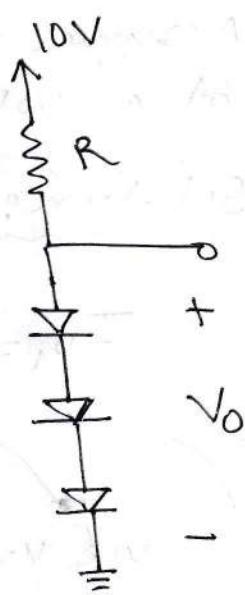
EX: 10, 11, 13 [Ch-2, BL, at the end of the chapter]  
29, 30, 31



### \* Half-wave rectifier

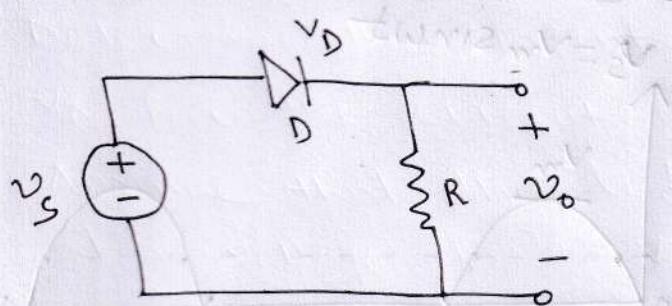


$$v_s = V_m \sin \omega t$$

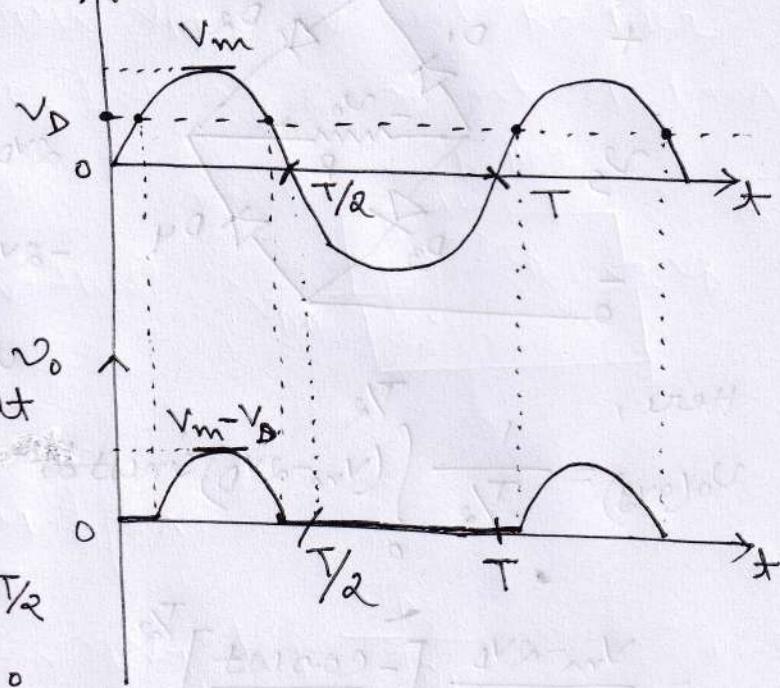

Here,



$$\begin{aligned}
 v_o(\text{avg.}) &= \frac{1}{T} \int_0^{T/2} (V_m - V_D) \sin \omega t dt \\
 &= \frac{V_m - V_D}{T} \left[ -\frac{\cos \omega t}{\omega} \right]_0^{T/2} \\
 &= \frac{V_m - V_D}{\omega T} \left[ \cos 0 - \cos \omega \frac{T}{2} \right] \\
 &= \frac{V_m - V_D}{\frac{2\pi}{T} \cdot T} \left[ 1 - \cos \frac{2\pi}{T} \cdot \frac{T}{2} \right] \\
 &= \frac{V_m - V_D}{2\pi} [1 + 1] \\
 &= \frac{V_m - V_D}{\pi} \\
 &= 0.318 (V_m - V_D).
 \end{aligned}$$

PIV

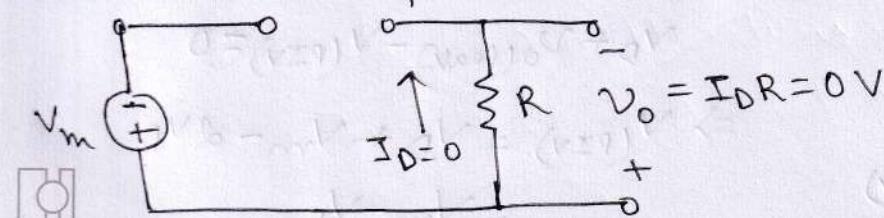

$$\therefore V_{(PIV)} = V_m.$$

## \* Full-wave (bridge) rectifier:

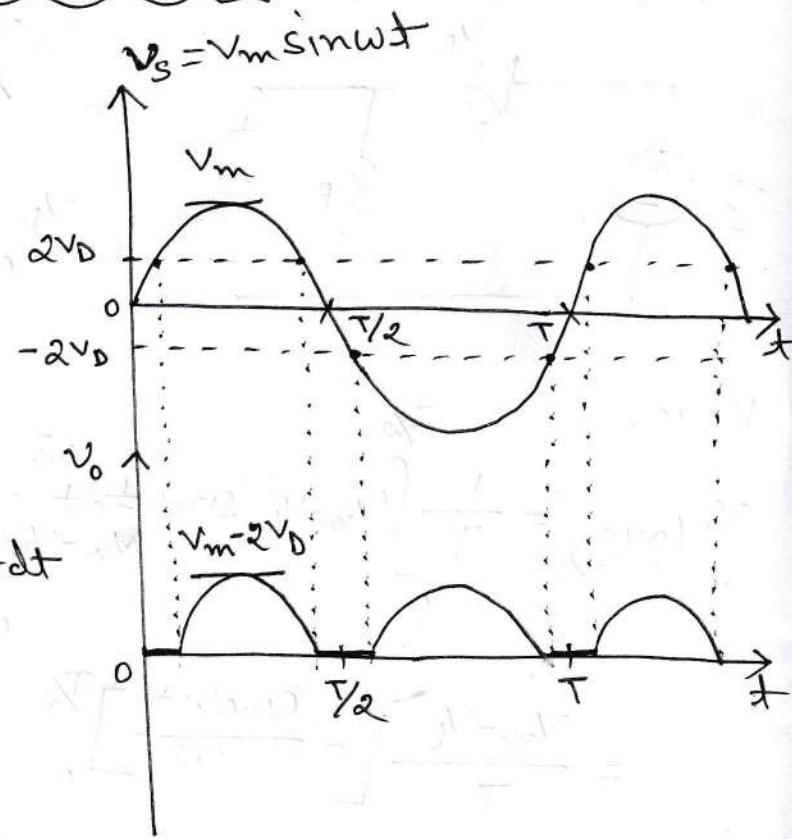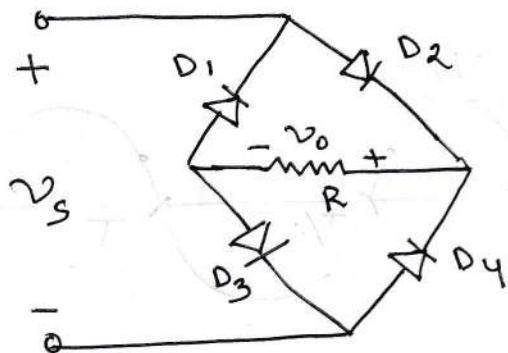

Here,

$$V_o(\text{avg}) = \frac{1}{T/2} \int_0^{T/2} (V_m - 2V_D) \sin \omega t dt$$

$$= \frac{V_m - 2V_D}{T/2} \left[ -\frac{\cos \omega t}{\omega} \right]_0^{T/2}$$


$$= \frac{V_m - 2V_D}{\omega T/2} \left[ \cos 0 - \cos \omega \frac{T}{2} \right]$$

$$= \frac{(V_m - 2V_D)}{\frac{2\pi}{T} \cdot \frac{T}{2}} \left[ 1 - \cos \frac{2\pi}{T} \cdot \frac{T}{2} \right]$$

$$= \frac{2(V_m - 2V_D)}{\pi}$$

$$= 0.636 (V_m - 2V_D).$$

PIV: Consider the positive half cycle

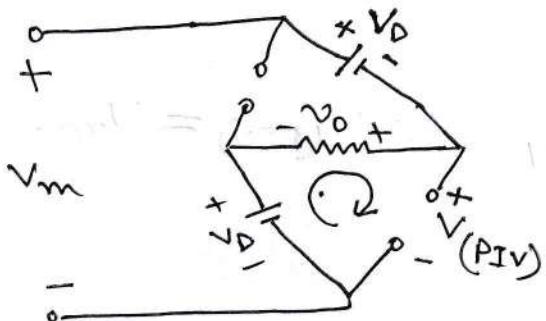



Apply KVL at the loop,

$$V_D + V_o(\text{peak}) - V(\text{PIV}) = 0$$

$$\Rightarrow V(\text{PIV}) = V_D + V_m - 2V_D \\ = V_m - V_D.$$


## \* Clippers

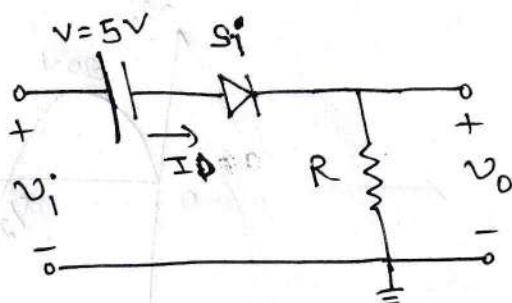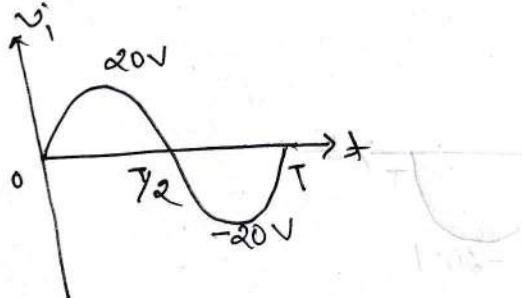Example 1: Sketch the output waveform of the network



Solution:

Transition voltage [ $I_D = 0$ ]

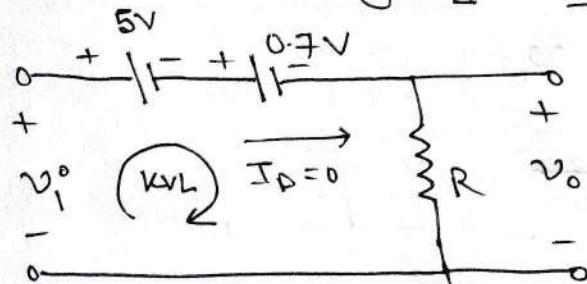


Apply KVL at the loop,

$$v_i - 5 - 0.7 \stackrel{I_D=0}{=} I_D R = 0$$

$$\Rightarrow v_i = 5.7 \text{ V}$$

Diode is in on-state, when


$$v_i > 5.7 \text{ V}$$

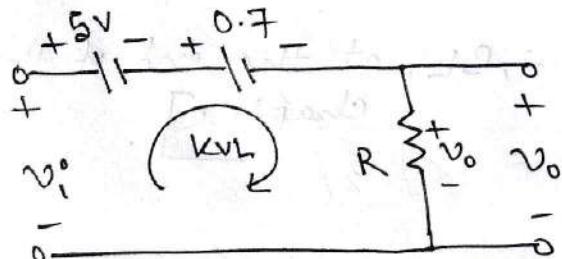


$$v_i - 5 - 0.7 - v_o = 0$$

$$\Rightarrow v_o = v_i - 5.7$$


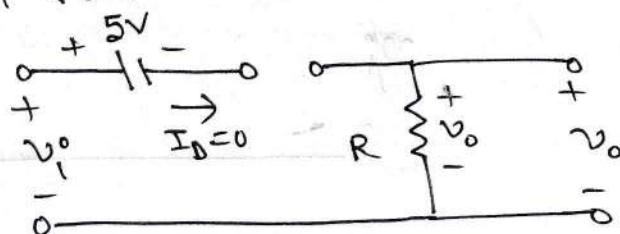
Diode is in off-state, when  
 $v_i < 5.7 \text{ V}$



$$\therefore v_o = 0$$

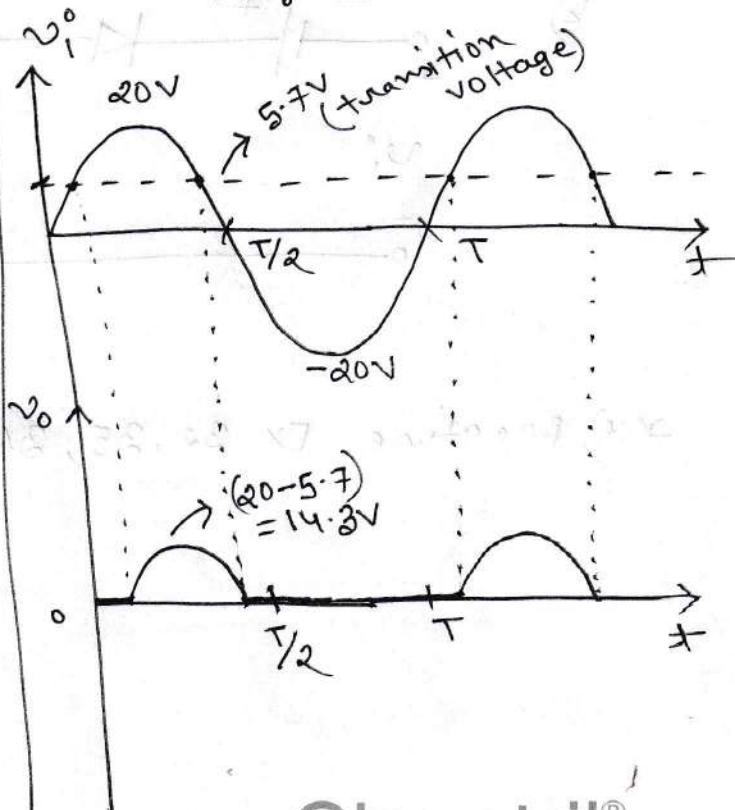


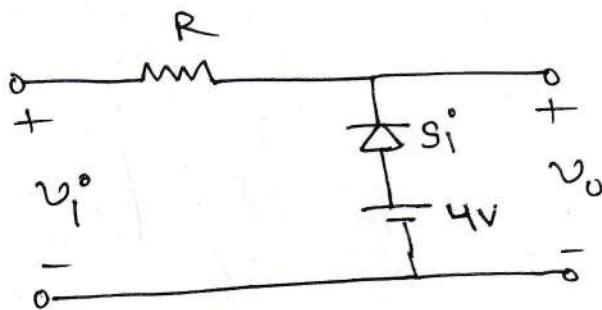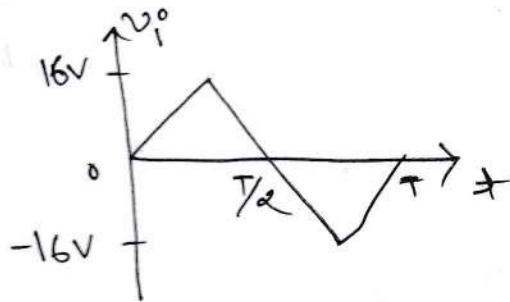Example 2: Determine  $v_o$  for the circuit



Solution:

Transition voltage [ $I_D = 0$ ]

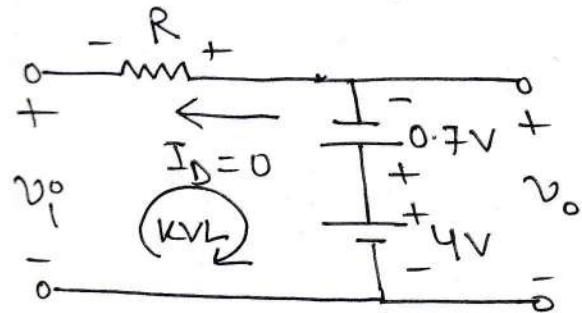

Apply KVL at the loop,


$$v_i^o + (0 \times R) + 0.7 - 4 = 0$$

$$\Rightarrow v_i^o - 3.3 = 0$$

$$\therefore v_i^o = 3.3V$$

Diode is in on-state, when


$$v_i^o < 3.3V$$

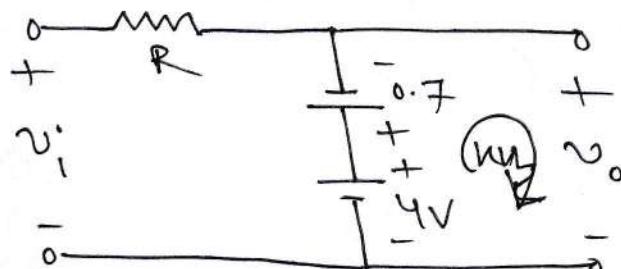


$$4 - 0.7 - v_o = 0$$

$$\Rightarrow v_o = 3.3V$$



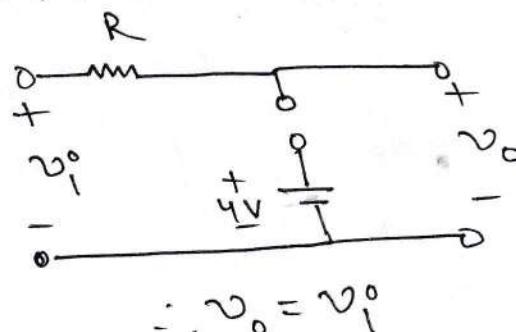
Diode is in off-state when  
 $v_i^o > 3.3V$



$$\therefore v_o = v_i^o$$

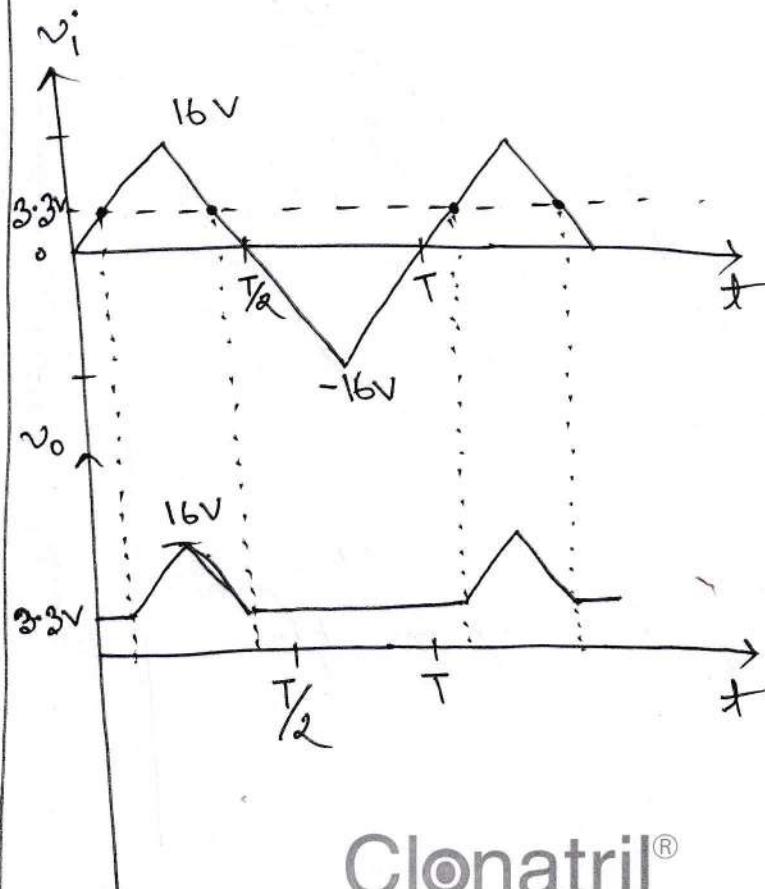

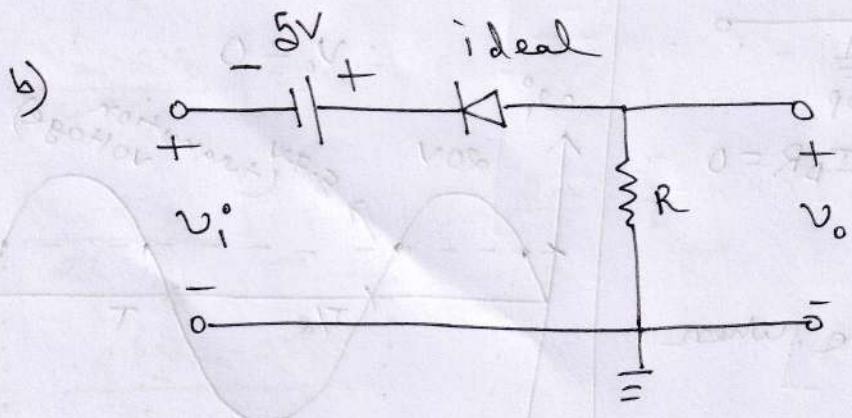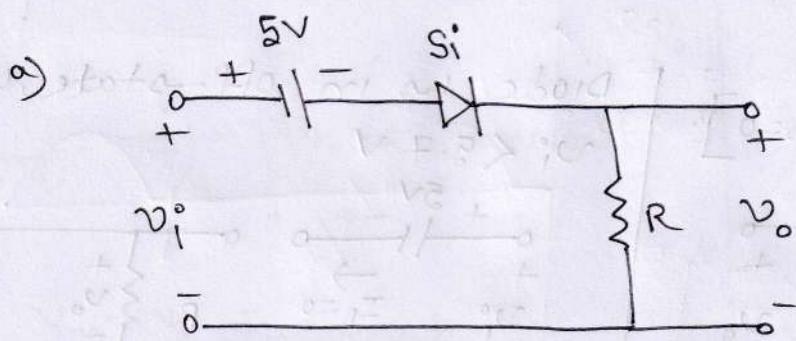
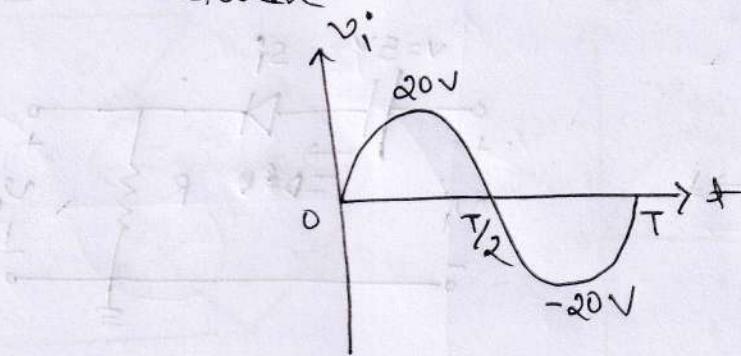
\*\*) Practise the following clippers circuit and sketch output waveform




\*\*) Practise EX 32, 35, 36 [Ch-2, BL, at the end of the chapter].

## \* Clampers

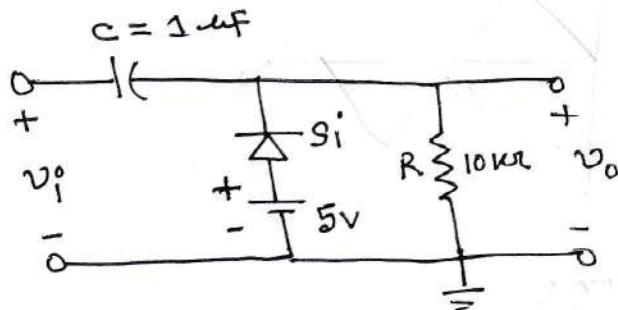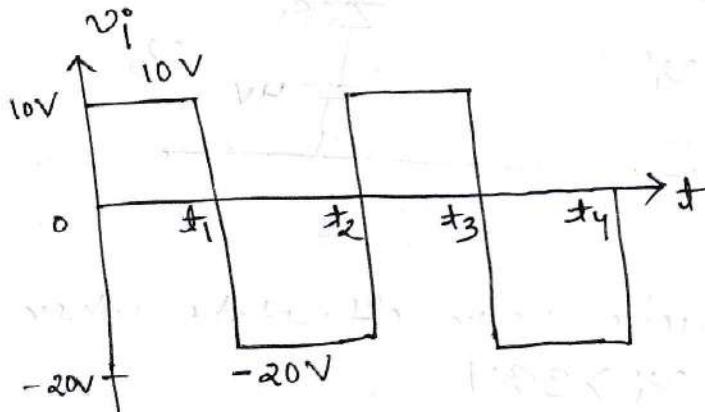Examples Determine  $v_o$  for the given network.



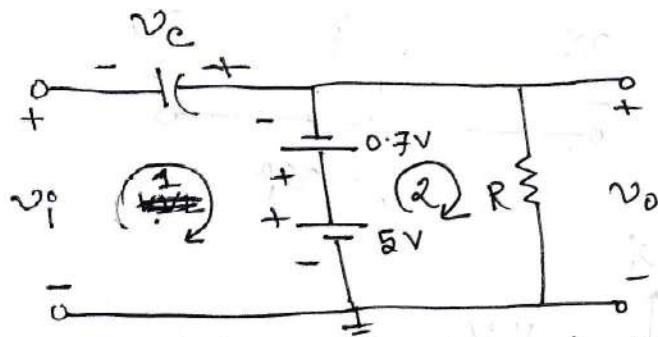Sol<sup>n</sup>: During the period  $t_1 \rightarrow t_2$ ,



Applying KVL at the loop 1,

$$v_i + v_c + 0.7 - 5 = 0$$

$$\Rightarrow -20 + v_c - 4.3 = 0$$


$$\therefore v_c = 24.3V$$

Apply KVL at loop 2,

$$5 - 0.7 - v_o = 0$$

$$\Rightarrow v_o = 4.3V$$


During the period  $t_2 \rightarrow t_3$

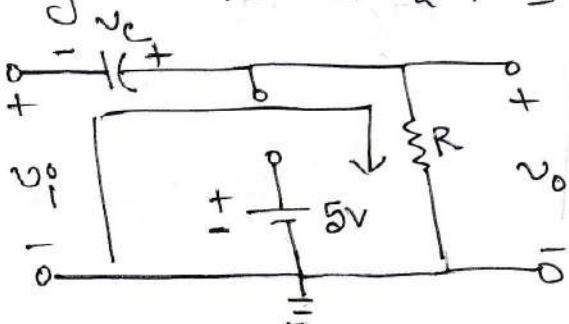




Apply KVL at the loop,

$$v_i + v_c - v_o = 0$$
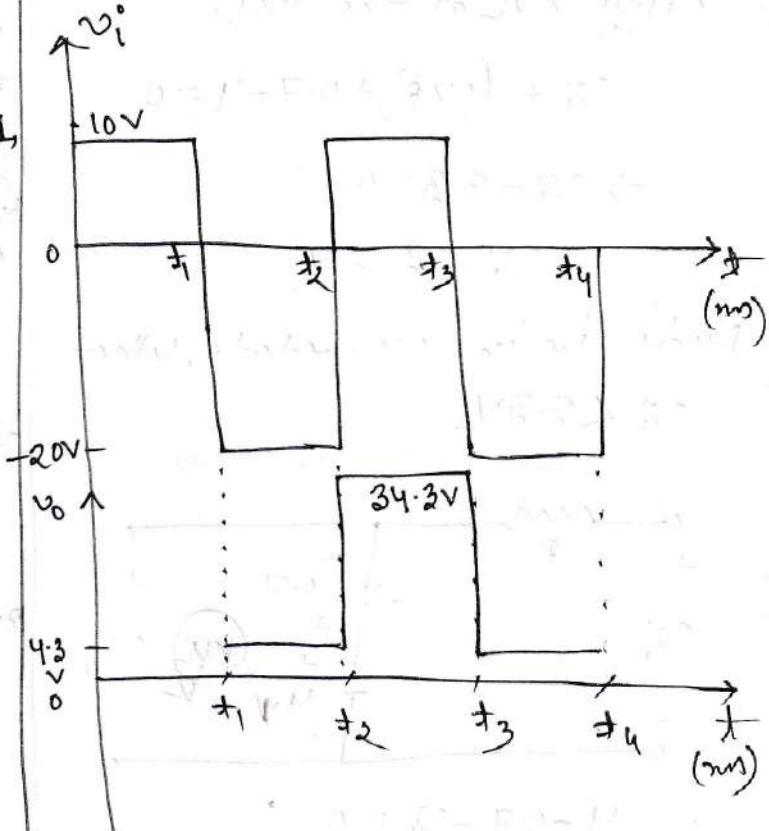
$$\begin{aligned} \Rightarrow v_o &= v_i + v_c \\ &= 0 - 20 + 4.3 \\ &= 34.3V \end{aligned}$$




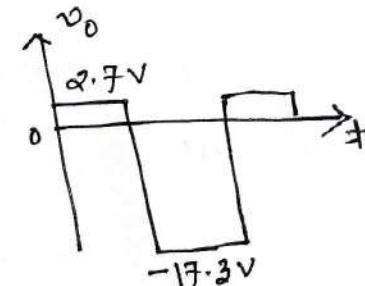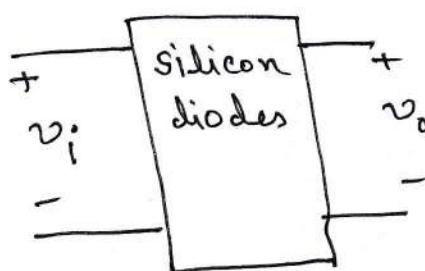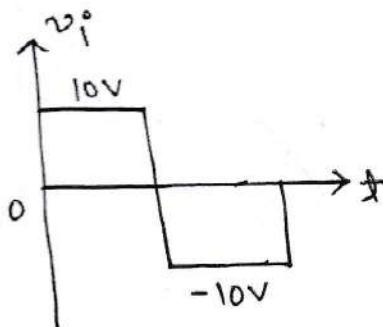Example: Design a clamer to perform the indicated in the network.




Sol: The required clamer circuit to generate the  $v_o$  is


$$C = 1\text{ nF}$$

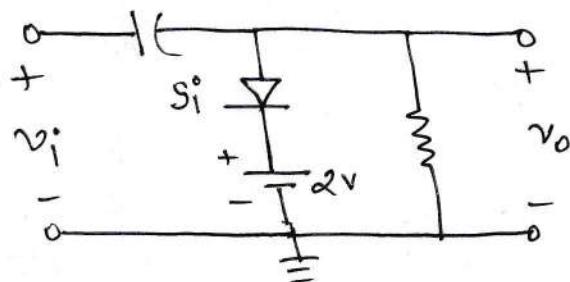

Justification:

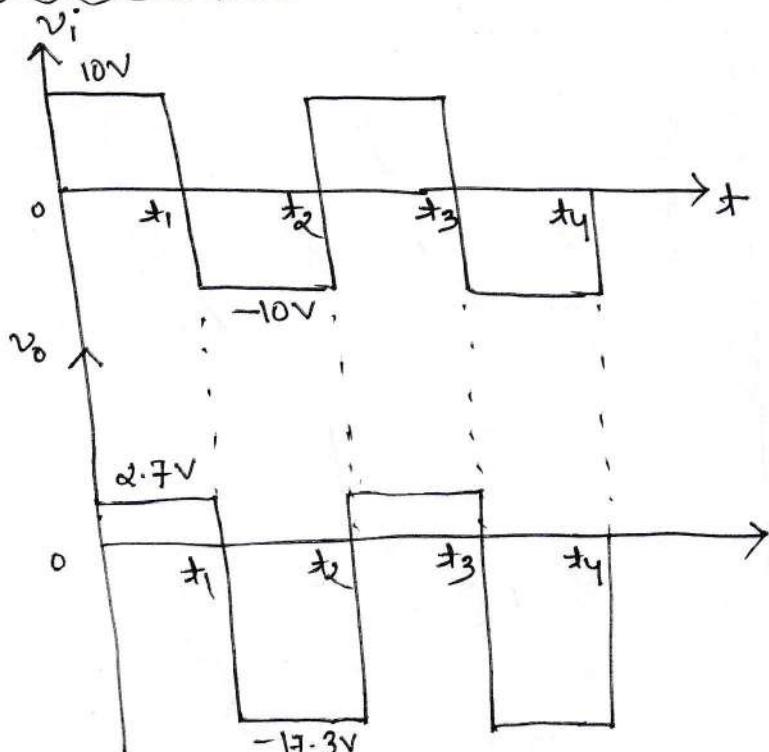

during the period  $0 \rightarrow t_1$

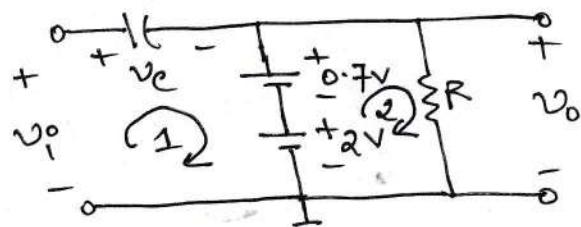

Apply KVL at loop 1,

$$v_i - v_c - 0.7 - 2 = 0$$

$$\Rightarrow v_c = v_i - 2.7$$


$$= 10 - 2.7 = 7.3\text{ V}$$

Apply KVL at loop 2,

$$2 + 0.7 - v_o = 0$$

$$\Rightarrow v_o = 2.7\text{ V}$$

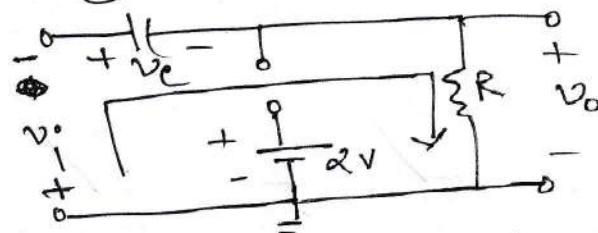during the period  $t_1 \rightarrow t_2$ ,



Apply KVL at the loop,

$$-v_i - v_c - v_o = 0$$

$$\Rightarrow v_o = -v_i - v_c = -10 - 7.3$$

**Clonatril®**

clonazepam

$$= -17.3\text{ V.}$$

### EX 4.28 (ch-4, SM)

For the circuit shown in Fig., both diodes are identical. Find the value of  $R$  for which  $V = 50\text{mV}$


Solution:

Here, diode  $D_1$  is in ON state

and "  $D_2$  " OFF "

$$\therefore R = \frac{V}{I} = \frac{50}{10} = 5\Omega.$$

(Ans.)

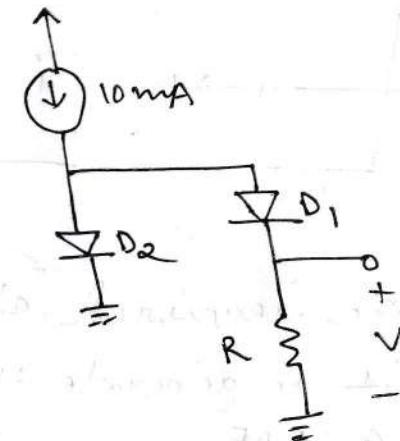

### EX: 4.58 (ch-4, SM)

Diode  $D_1$  &  $D_2$  are 10 mA units, that is, each has a voltage drop of 0.7 V at a current of 10 mA. Use ~~its~~ constant voltage drop model to find  $V_o$  with the  $150\Omega$  load connected.


Sol<sup>n</sup>:

Here,

$$V_o = 0.7 + 0.7$$

$$= 1.4\text{V}.$$

(Ans.)

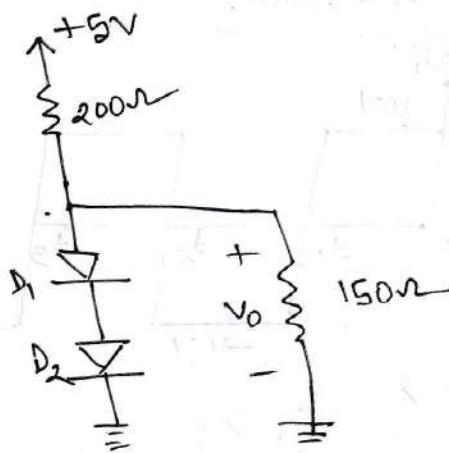

\* Practice: 37, 39(c), 40, 41, 42. (Ch-2, BL)

4.35 (ch-4, SM)

use the iterative analysis to determine the diode current and voltage of Fig. for  $V_{DD} = 1V$ ,  $R = 1\text{ k}\Omega$ , and  $I_S = 10^{-15} \text{ A}$ .


(4.10)

Sol<sup>m</sup>: To begin the iteration,

we assume,  $V_D = 0.7 \text{ V}$

$$\therefore I_D = I_S e^{\frac{V_D}{V_T}} = 10^{-15} \times e^{\frac{0.7}{0.025}}$$

$$= 1.44 \text{ mA}$$

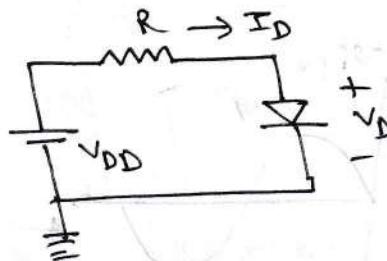

From the circuit,

$$I_D = \frac{V_{DD} - V_D}{R} = \frac{1 - 0.7}{1} = 0.3 \text{ mA}$$

We know,

$$V_{D2} - V_{D1} = 2.3 V_T \log \left( \frac{I_{D2}}{I_{D1}} \right)$$
$$\Rightarrow V_{D2} - 0.7 = 2.3 \times 0.025 \times \log \left( \frac{0.3}{1.44} \right)$$
$$\Rightarrow V_{D2} - 0.7 = -0.0392$$

$$\Rightarrow V_{D2} = 0.6608 \text{ V}$$

Again from the circuit,  $I_D = \frac{V_{DD} - V_D}{R} = \frac{1 - 0.6608}{1} = 0.3392 \text{ mA}$

Again,



$$V_{D3} - V_{D2} = 2.3 V_T \log \left( \frac{I_{D3}}{I_{D2}} \right)$$
$$\Rightarrow V_{D3} - 0.6608 = 2.3 \times 0.025 \times \log \left( \frac{0.3392}{0.3} \right)$$

$$\Rightarrow V_{D3} - 0.6608 = -0.003$$

$$\therefore V_{D3} = 0.6638 \text{ V}$$


Do another one or two more iterations and write the answers.

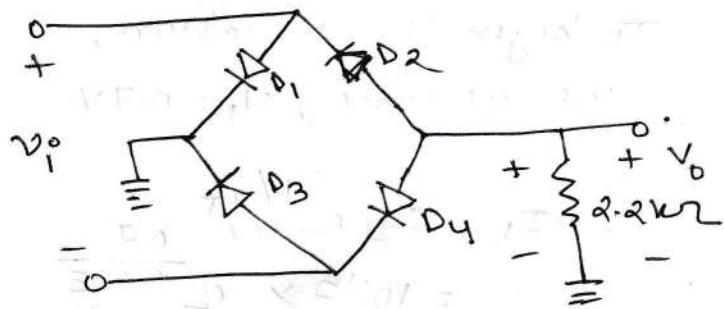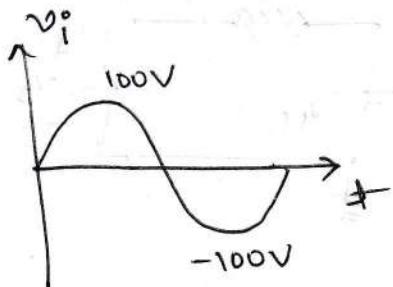Ex 29 (Ch-2, BL) Determine  $v_o$  and PIV of the fig.




Sol<sup>n</sup>: During the positive half cycle, diodes  $D_1$  &  $D_4$  are ON.

$$\therefore v_o = -v_i$$

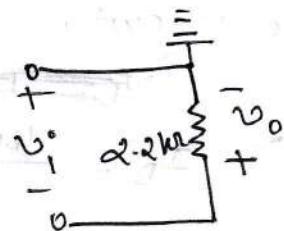


During the negative half cycle, diodes  $D_2$  &  $D_3$  are ON


$$\therefore v_o = -v_i$$

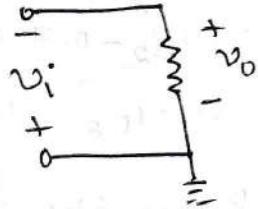

Waveform:

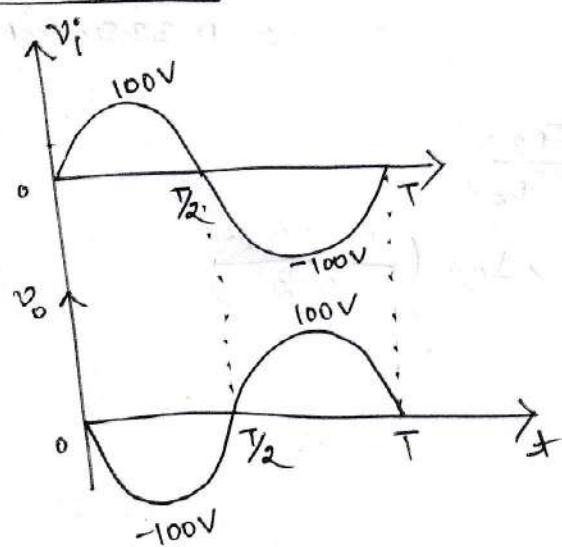

PIV $v_o$

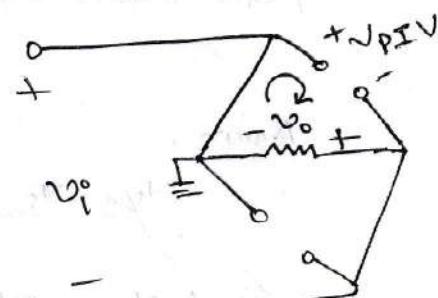


Apply KVL,

$$-v_{\text{PIV}} - v_o(\text{peak}) = 0$$


$$\Rightarrow v_{\text{PIV}} = -v_o(\text{peak}) \\ = -100\text{V}.$$

(Ans.)

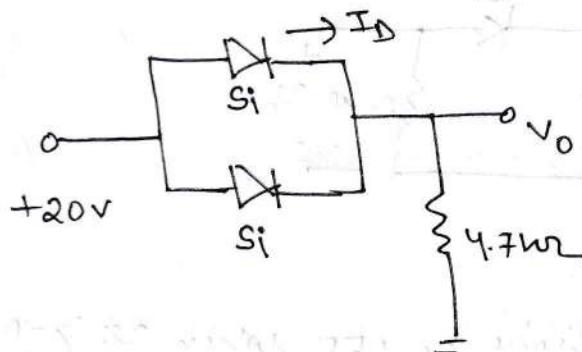Ex 10 (ch-2, BL): Determine  $V_o$  and  $I_D$  for the networks.




(a)

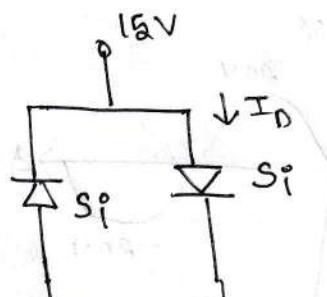

(b)

Sol:

(a)

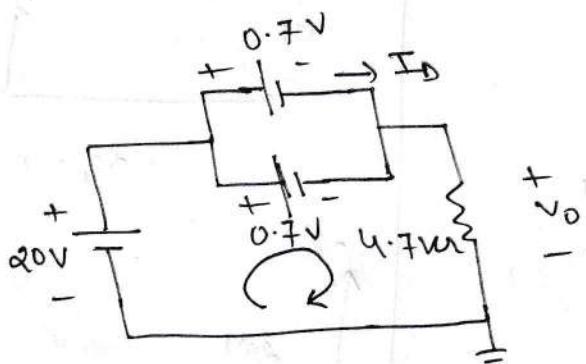

$$\text{Apply KVL, } 20 - 0.7 - V_o = 0$$

$$\Rightarrow V_o = 19.3 \text{ V}$$

$$\therefore I_{4.7k\Omega} = \frac{V_o}{4.7} = \frac{19.3}{4.7} = 4.11 \text{ mA.}$$


$$\therefore I_D = \frac{I_{4.7k\Omega}}{2} = 2.055 \text{ mA.} \quad (\text{Ans.})$$

b) Here,



$$V_o = 15 - 0.7 \\ = 14.3 \text{ V}$$

$$\text{and } I_D = \frac{15 + 5 - 0.7}{2.2} \\ = 8.77 \text{ mA.}$$


(Ans.)

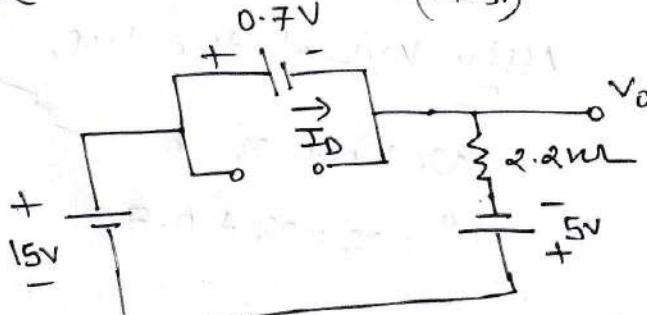

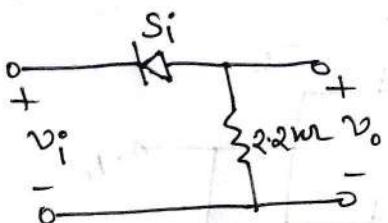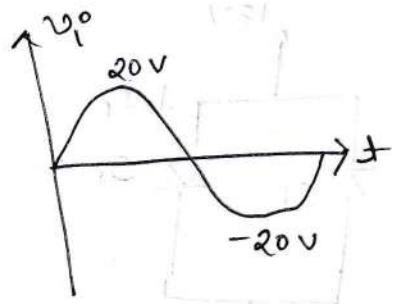32). (Ch-2, Bm) Determine  $v_o$  for the network.



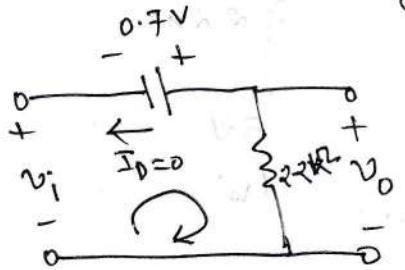Sol<sup>m</sup> Transition voltage ( $I_D=0$ )




Apply KVL at the loop,

$$v_i + 0.7 - (2.2 \times I_D) = 0$$

$$\Rightarrow v_i = -0.7$$

Diode is ON when  $v_i < -0.7V$

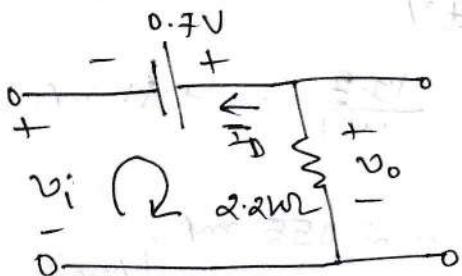


Apply KVL at the loop,


$$v_i + 0.7 - v_o = 0$$

$$\therefore v_o = v_i + 0.7$$


Diode is OFF when  $v_i > -0.7V$

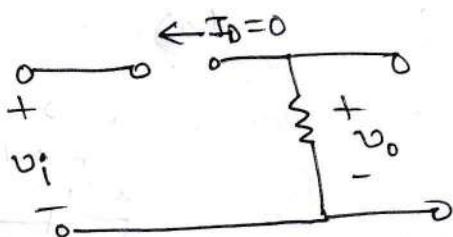


$$\therefore v_o = 0$$

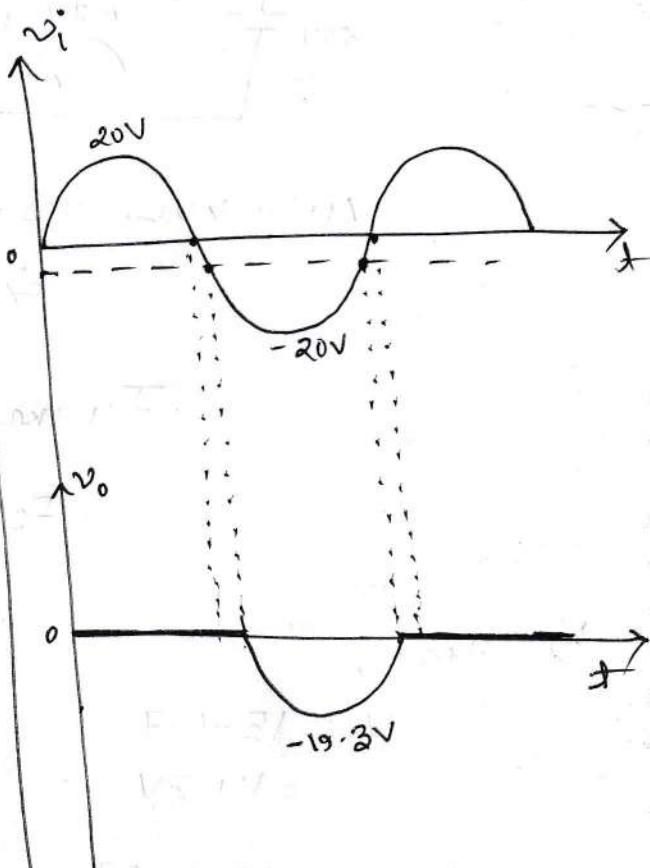

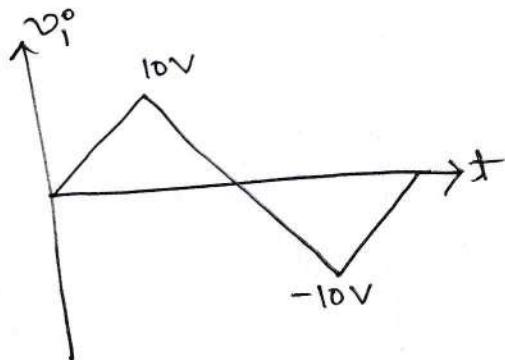
36 (Ch-2, BL) : Sketch  $v_o$  for the network



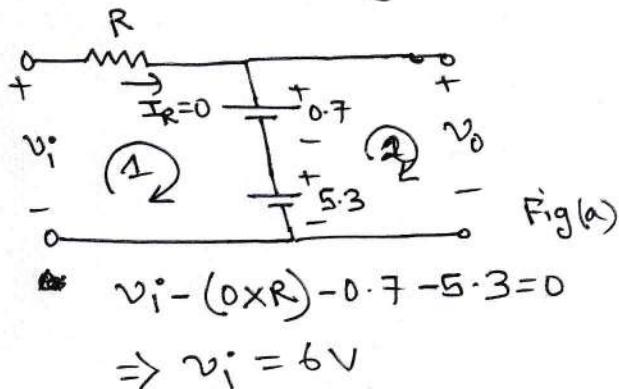Sol<sup>n</sup>: For the diode  $D_1$ , the transition voltage is,




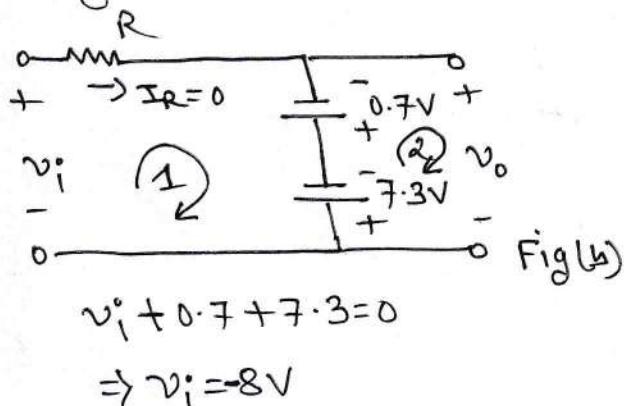For the diode  $D_2$ , the transition voltage is,



When  $v_i > 6V$ , diode  $D_1$  is ON and  $D_2$  is OFF. Apply KVL at the loop 2 in Fig(a),

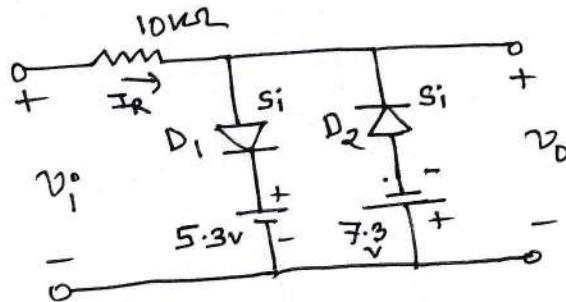
$$5.3 + 0.7 - v_o = 0$$
 $\Rightarrow v_o = 6V$




when  $v_i < -8V$ , the diode  $D_1$  is OFF and  $D_2$  is ON. Apply KVL at the loop 2 in Fig(b),

$$-7.3 - 0.7 - v_o = 0$$
 $\Rightarrow v_o = -8V$

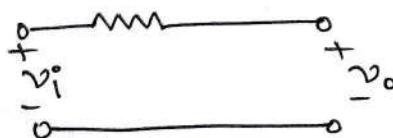when  $-8V < v_i < 6V$ , both  $D_1$  &  $D_2$  are OFF.  $R = 10k\Omega$



$$\therefore v_o = v_i$$

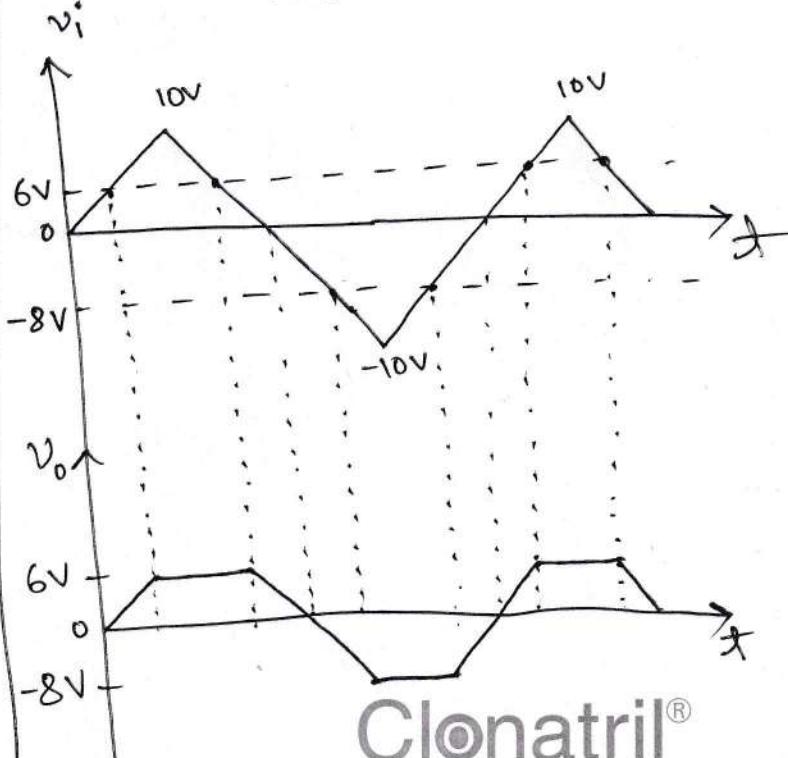



# BJT

Example 6.4 (P-335)

Analyse this circuit to determine all node voltages and branch currents.  $\beta = 100$ .

~~Soln~~

Soln: Redraw the circuit,

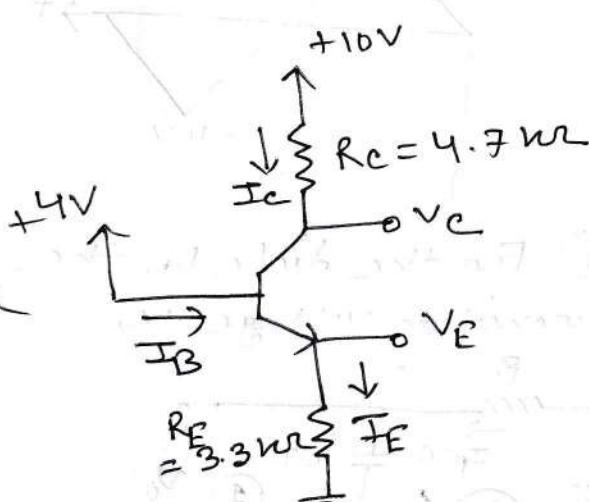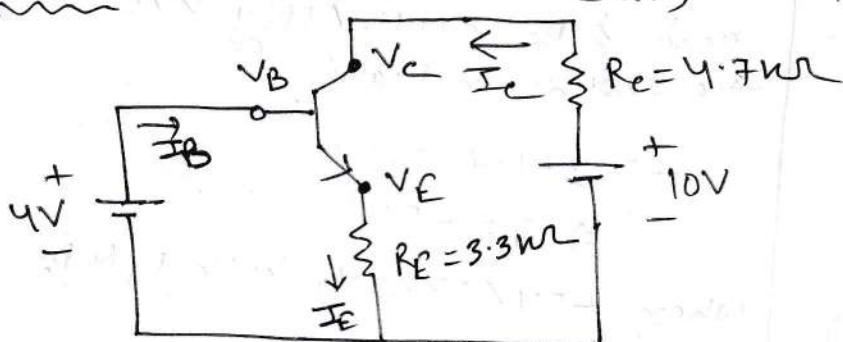

$$\text{Here, } V_B = 4V$$

$$\text{we know, } V_{BE} = 0.7V$$

$$\Rightarrow V_B - V_E = 0.7$$

$$\Rightarrow V_E = V_B - 0.7 = 4 - 0.7 = 3.3V$$

$$\therefore I_E = \frac{V_E}{R_E} = \frac{3.3}{3.3} = 1mA$$

we know,

$$I_E = I_B + I_C$$

$$\Rightarrow I_E = I_B + \beta I_B \quad [\because \beta = \frac{I_C}{I_B}]$$

$$\Rightarrow I_B = \frac{I_E}{\beta + 1} = \frac{1}{101} = 0.0099 \text{ mA}$$

$$\therefore I_C = \beta I_B = 100 \times 0.0099 = 0.99 \text{ mA}$$


$$\therefore V_C = 10 - I_C R_C = 10 - (0.99 \times 4.7) = 5.3V$$

→ X →

### Example 6.7 (P-339)

Determine the voltages at all nodes and the currents through all branches. Assume,  $\beta = 100$ .

Soln:

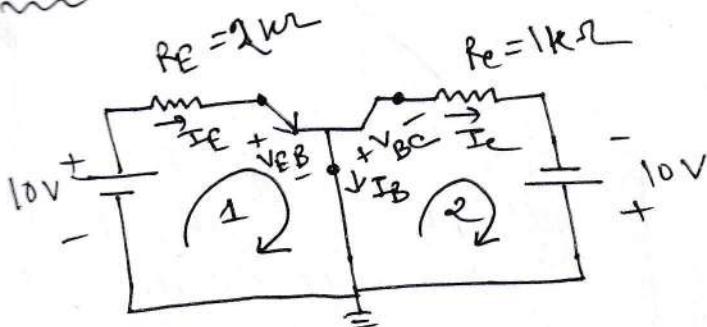

Apply KVL at loop 1,

$$10 - I_E R_E - V_{EB} = 0$$

$$\Rightarrow I_E = \frac{10 - 0.7}{2} = 4.65 \text{ mA}$$

$$\therefore I_B = \frac{I_E}{\beta + 1} = \frac{4.65}{101} \approx 0.046 \text{ mA}$$

$$\therefore I_C = \beta I_B = 100 \times 0.046 = 4.6 \text{ mA}$$

$$V_B = 0 \text{ V}$$

$$\therefore V_E = V_{EB} + V_B = 0.7 + 0 = 0.7 \text{ V}$$

Apply KVL at loop 2,

$$-V_{BC} - I_C R_C + 10 = 0$$

$$\Rightarrow V_{BC} = 10 - (4.6 \times 1) = 5.4$$

$$\Rightarrow V_B - V_C = 5.4$$

$$\Rightarrow V_C = -5.4 \text{ V}$$

(Ans.)

**Clonatril®**  
clonazepam



Practice:


Example 6.4, 6.8

Exercise 6.29, 6.32, 6.34, 6.51, 6.56

Op amp

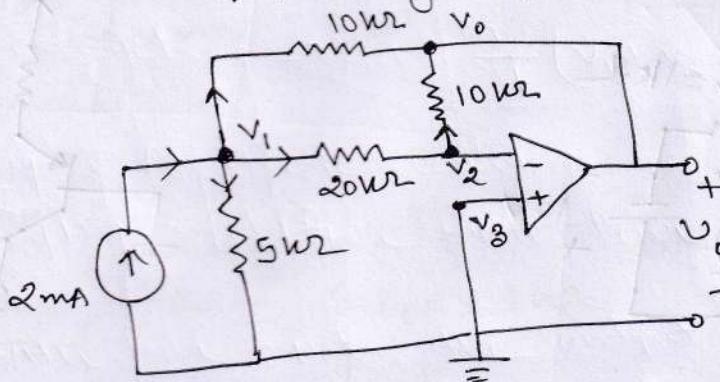Exercise 5.44 (P-203)

Determine the output voltage  $v_o$  in the circuit.



Sol<sup>n</sup>: Apply nodal analysis at node 2,

$$\frac{v_1 - v_2}{20} = \frac{v_2 - v_o}{10}$$

$$\Rightarrow \frac{v_1}{20} = -\frac{v_o}{10} \quad [ \because v_2 = v_3 = 0 ]$$

$$\Rightarrow v_1 = -2v_o \quad (i)$$

Apply nodal analysis at node 1,

$$2 = \frac{v_1}{5} + \frac{v_1 - v_2}{20} + \frac{v_1 - v_o}{10}$$

$$\Rightarrow 2 = \frac{-2v_o}{5} - \frac{2v_o}{20} - \frac{3v_o}{10} \quad [ \text{from (i)} ]$$

$$\Rightarrow 2 = \frac{-8v_o - 2v_o - 6v_o}{20}$$

$$\Rightarrow -16v_o = 40$$

$$\Rightarrow v_o = -\frac{40}{16}$$


$$\therefore v_o = -\frac{5}{2} \text{ V.}$$

(Ans.)

Practice: 5.19, 5.20.

Ex 5.31 (P-205)

For the circuit, determine  $i_x$ .

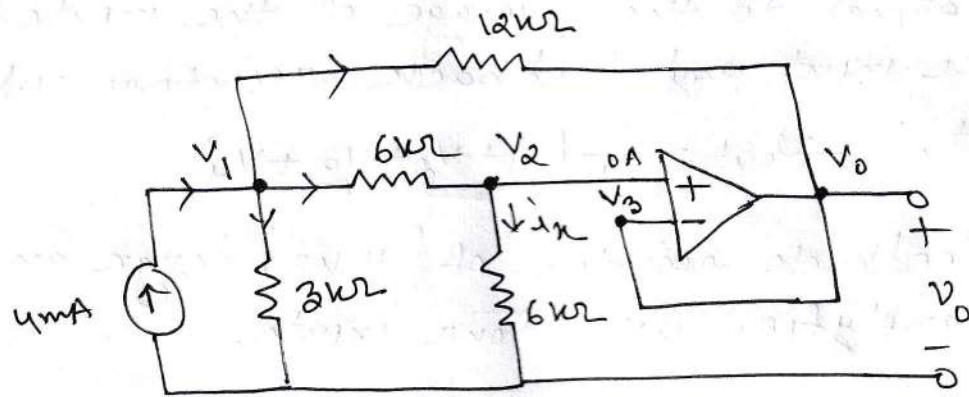

Sol<sup>n</sup>

Apply nodal analysis at node 2,

$$\frac{V_1 - V_2}{6} = \frac{V_2}{6}$$

$$\Rightarrow \frac{V_1 - V_0}{6} = \frac{V_0}{6} \quad [\because V_2 = V_3 = V_0]$$

$$\Rightarrow \frac{V_1}{6} = \frac{2V_0}{6}$$

$$\therefore V_1 = 2V_0 \quad (i)$$

Apply nodal analysis at node 1,

$$4 = \frac{V_1}{3} + \frac{V_1 - V_2}{6} + \frac{V_1 - V_0}{12}$$

$$\Rightarrow 4 = \frac{2V_0}{3} + \frac{2V_0 - V_0}{6} + \frac{2V_0 - V_0}{12}$$

$$\Rightarrow 4 = \frac{2V_0}{3} + \frac{V_0}{6} + \frac{V_0}{12}$$

$$\Rightarrow 4 = \frac{8V_0 + 2V_0 + V_0}{12}$$

$$\Rightarrow 11V_0 = 48$$

$$\Rightarrow V_0 = \frac{48}{11}$$

$$\therefore i_x = \frac{V_2}{6} = \frac{V_0}{6} = \frac{48}{11 \times 6} = \frac{8}{11} \text{ mA. (Ans.)}$$

Ex 5.41 (P-207)

An averaging amplifier is a summer that provides an output equal to the average of the inputs. By using proper input and feedback resistors values, one can get,  $-V_{out} = \frac{1}{4} (V_1 + V_2 + V_3 + V_4)$

using a feedback resistor of  $10\text{k}\Omega$ , design an averaging amplifier with four inputs.

So<sup>Mo</sup> with four inputs, the output of a summer is,

$$V_{out} = - \left( \frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 + \frac{R_f}{R_4} V_4 \right) \quad \text{--- (i)}$$

Given,

$$-V_{out} = \frac{1}{4} (V_1 + V_2 + V_3 + V_4)$$



$$\Rightarrow V_{out} = - \left( \frac{1}{4} V_1 + \frac{1}{4} V_2 + \frac{1}{4} V_3 + \frac{1}{4} V_4 \right) \quad \text{--- (ii)}$$

Comparing eqn (i) & (ii) we get,

$$\frac{R_f}{R_1} = \frac{R_f}{R_2} = \frac{R_f}{R_3} = \frac{R_f}{R_4} = \frac{1}{4}$$

If  $R_f = 10\text{k}\Omega$ , then,  $R_1 = R_2 = R_3 = R_4 = 4 \times R_f = 40\text{k}\Omega$

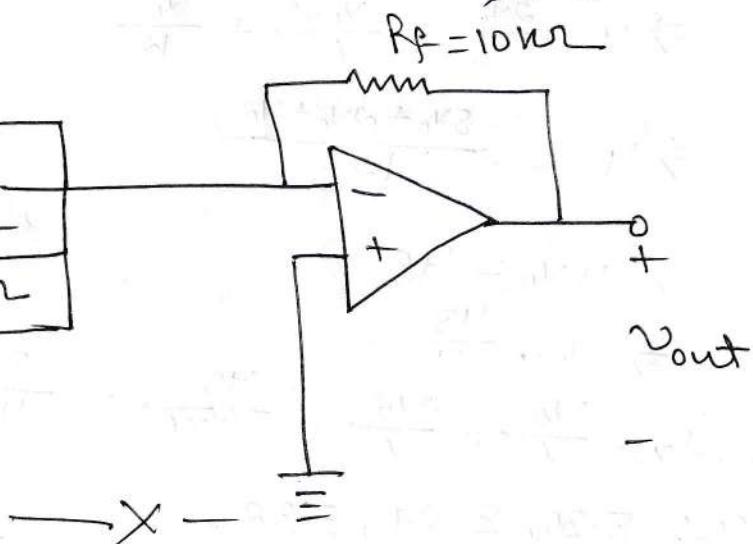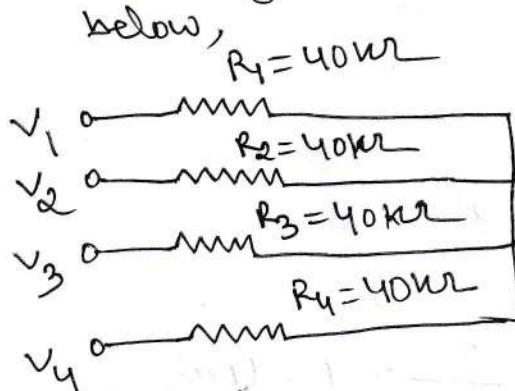The designed circuit of the averaging amplifier is given below,



Practice: 5.42, 5.43

Ex 5.46 (P-207)

using only two op amps, design a circuit to solve

$$-v_{out} = \frac{v_1 - v_2}{3} + \frac{v_3}{2}$$

Sol<sup>n</sup>: Given,


$$-v_{out} = \frac{v_1 - v_2}{3} + \frac{v_3}{2}$$

$$\Rightarrow v_{out} = -\left(\frac{1}{3}v_1 - \frac{1}{3}v_2 + \frac{1}{2}v_3\right)$$

$$\Rightarrow v_{out} = -\left[\frac{1}{3}v_1 + \frac{1}{3}(-v_2) + \frac{1}{2}v_3\right]$$

$$\Rightarrow v_{out} = -\left[\frac{R}{3R}v_1 + \frac{R}{3R}\left(-\frac{R}{R}\right)v_2 + \frac{R}{2R}v_3\right]$$


Therefore, the designed circuit is,

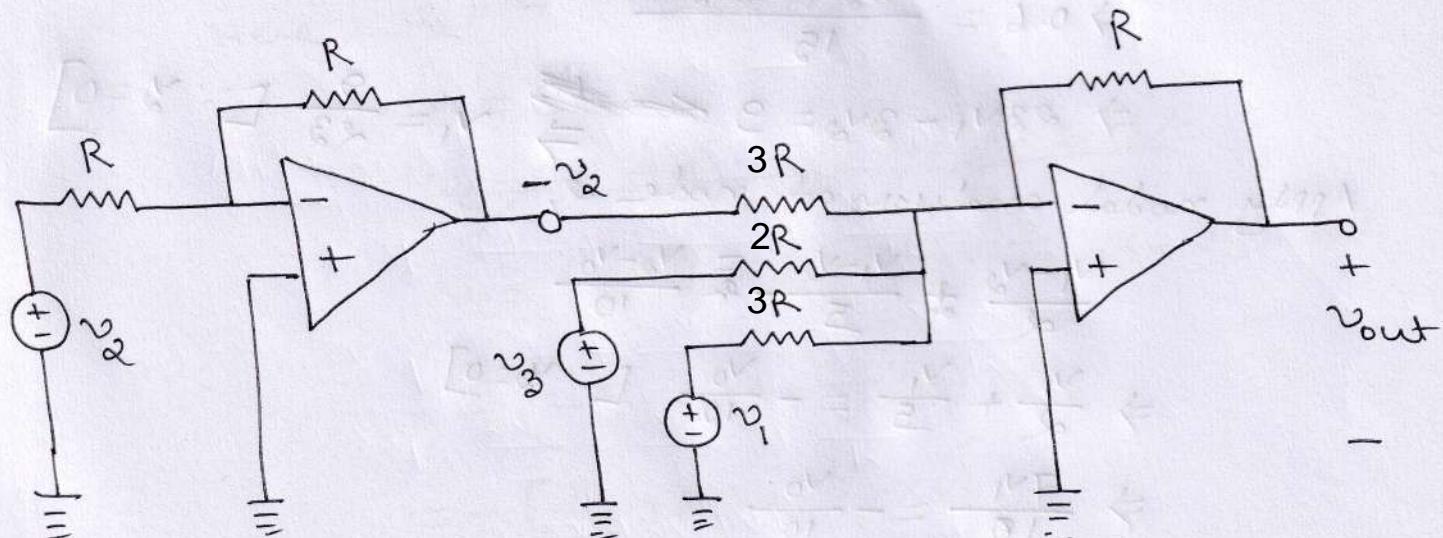

Practice: 5.45, 5.49, 5.50

Ex 5.58 (P-209)

Calculate  $i_o$  in the op amp circuit.

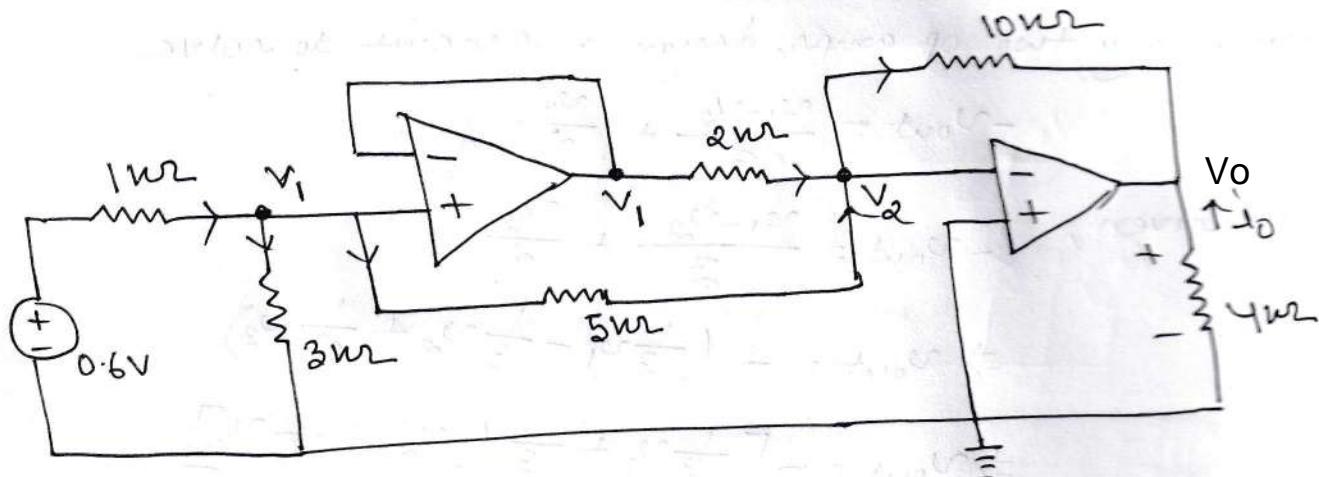

Sol<sup>n</sup>: Apply nodal analysis at node 1,

$$\frac{0.6 - v_1}{1} = \frac{v_1}{3} + \frac{v_1 - v_2}{5}$$

$$\Rightarrow 0.6 = v_1 + \frac{v_1}{3} + \frac{v_1}{5} - \frac{v_2}{5}$$

$$\Rightarrow 0.6 = \frac{23v_1 - 3v_2}{15}$$

$$\Rightarrow 23v_1 - 3v_2 = 9 \quad \cancel{\Rightarrow} \quad v_1 = \frac{9}{23} \quad [\because v_2 = 0]$$

Apply nodal analysis at node 2,

$$\frac{v_1 - v_2}{2} + \frac{v_1 - v_2}{5} = \frac{v_2 - v_o}{10}$$

$$\Rightarrow \frac{v_1}{2} + \frac{v_1}{5} = -\frac{v_o}{10} \quad [\because v_2 = 0]$$

$$\Rightarrow \frac{7v_1}{10} = -\frac{v_o}{10}$$


$$\Rightarrow v_o = -7v_1$$

$$\Rightarrow v_o = -7 \times \frac{9}{23} = -\frac{63}{23}$$

$$\therefore i_o = -\frac{v_o}{4} = \frac{63}{4 \times 23} = \frac{63}{92} = 0.685 \text{ mA.}$$

(Ans.)

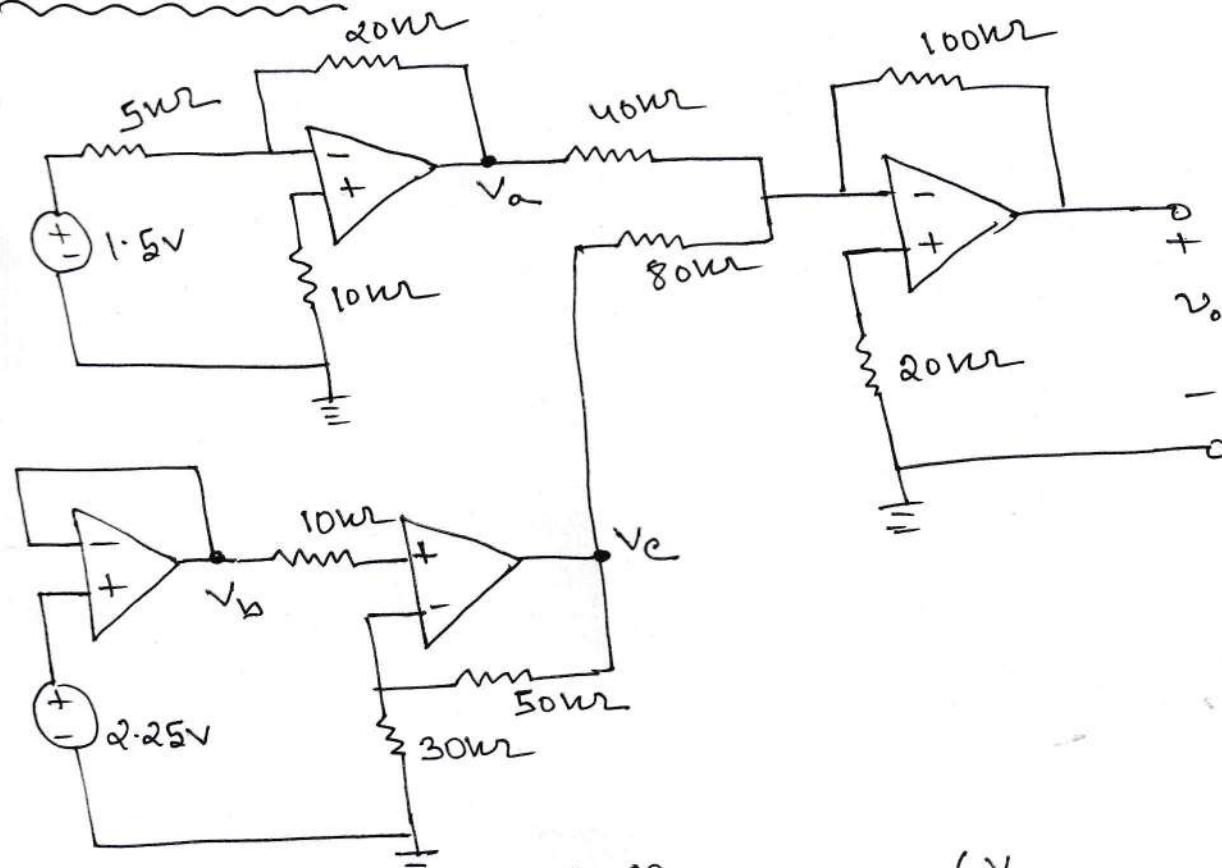Ex 5.71 (P-211) Determine  $v_o$  in the op amp circuit.



$$\text{Soln: Here, } v_a = - \left( \frac{20}{5} \right) \times 1.5 = -6 \text{ V}$$

$$v_b = 2.25 \text{ V}$$

~~$$v_c = - \left( \frac{50}{30} \right) \times 2.25 = - \frac{5}{3} \times 2.25 =$$~~

$$v_c = \left( 1 + \frac{50}{30} \right) v_b = \left( 1 + \frac{5}{3} \right) \times 2.25 = 6 \text{ V}$$

$$\therefore v_o = - \left( \frac{100}{40} v_a + \frac{100}{80} v_c \right)$$


$$= - \left[ \frac{10}{4} \times (-6) + \frac{10}{8} \times 6 \right]$$

$$= 15 - 7.5$$

$$= 7.5 \text{ V. (Ans.)}$$

Practice: 5.65, 5.68, 5.67, 5.74

## Integrator

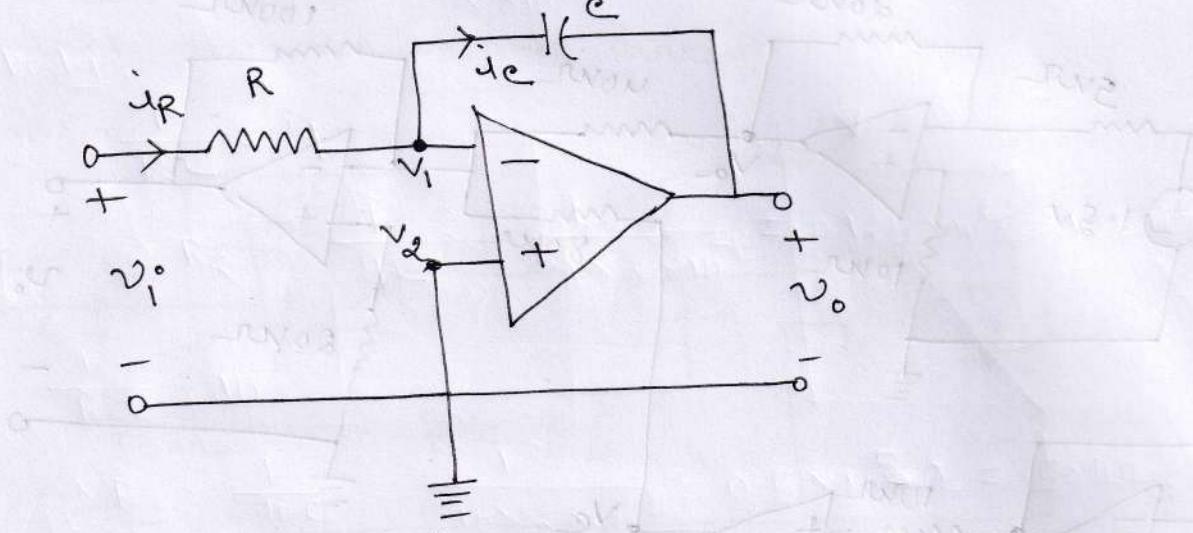

$$\text{Here, } i_R = i_C$$

$$\Rightarrow \frac{v_o - v_1}{R} = -C \frac{dv_1}{dt}$$

$$\Rightarrow \frac{v_o - v_1}{R} = -C \frac{d}{dt} (v_i - v_o)$$

$$\Rightarrow \frac{v_i}{R} = -C \frac{dv_o}{dt} \quad [ \because v_1 = v_2 = 0 ]$$


$$\Rightarrow \frac{dv_o}{dt} = -\frac{1}{RC} v_i$$

$$\therefore v_o = -\frac{1}{RC} \int v_i dt$$

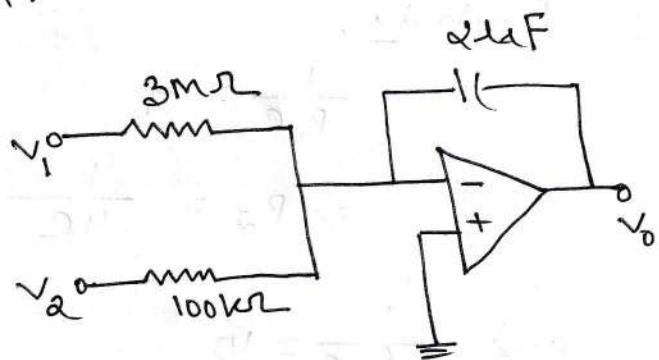Example 6.13 (P-235) If  $v_1 = 10 \cos 2t \text{ mV}$  and  $v_2 = 0.5 t \text{ mV}$  find  $v_o$  in the op amp circuit.

Soln:

$$v_o = - \left[ \frac{1}{R_1 C} \int v_1 dt + \frac{1}{R_2 C} \int v_2 dt \right]$$



$$\begin{aligned}
 &= - \left[ \frac{1}{3 \times 10^3 \times 2 \times 10^{-6}} \int 10 \cos 2t dt + \frac{1}{100 \times 10^3 \times 2 \times 10^{-6}} \int 0.5 t dt \right] \\
 &= - \frac{10}{6} \left[ \frac{\sin 2t}{2} \right] - \frac{0.5}{0.2} \left[ \frac{t^2}{2} \right] \\
 &= [ -0.833 \sin 2t - 1.25 t^2 ] \text{ mV. (Ans.)}
 \end{aligned}$$

Ex 6.71 (P-250): Show how you would use a single op amp to generate  $v_o = - \int^t (v_1 + 4v_2 + 10v_3) dt$ . If the integrating capacitor is  $C = 2 \mu\text{F}$ , obtain the other component values.

Soln: Using a single op amp, the integrator circuit's output with three input signals is,

$$v_o = - \left[ \frac{1}{R_1 C} \int v_1 dt + \frac{1}{R_2 C} \int v_2 dt + \frac{1}{R_3 C} \int v_3 dt \right] \quad \text{--- (i)}$$

Given,  $v_o = - \int^t [v_1 + 4v_2 + 10v_3] dt \quad \text{--- (ii)}$

Comparing (i) with (ii) we have,

$$\frac{1}{R_1 C} = 1$$

$$\Rightarrow R_1 = \frac{1}{C} = \frac{1}{2 \times 10^{-6}} = 0.5 \times 10^6 \Omega = 500 \text{ k}\Omega$$

Similarly,


$$\frac{1}{R_2 C} = 4$$

$$\Rightarrow R_2 = \frac{1}{4C} = \frac{1}{4 \times 2 \times 10^{-6}} = 0.125 \times 10^6 \Omega = 125 \text{ m}\Omega$$


$$\text{and } \frac{1}{R_3 C} = 10$$

$$\Rightarrow R_3 = \frac{1}{10C} = \frac{1}{10 \times 2 \times 10^{-6}} = 0.5 \times 10^5 \Omega = 50 \text{ k}\Omega$$

Therefore, the designed circuit is,

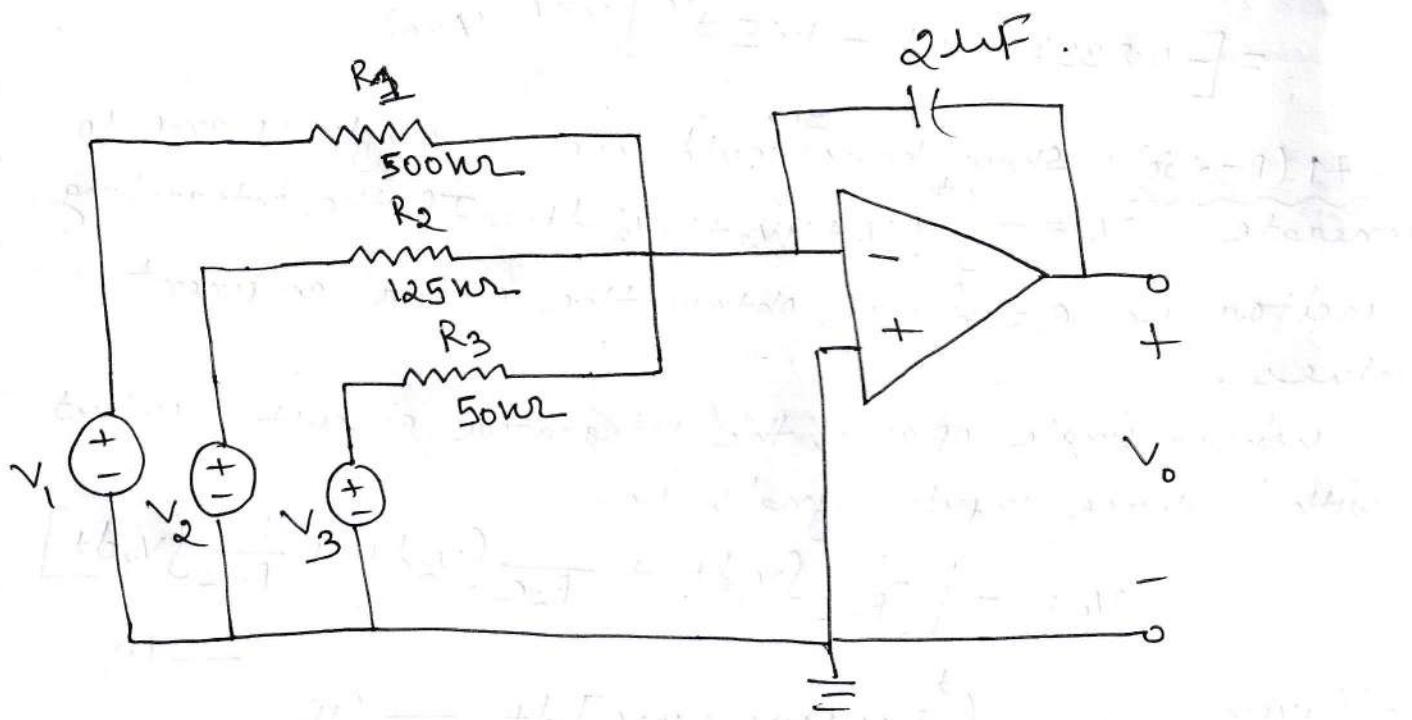

practise: 6.67, 6.70, 6.72

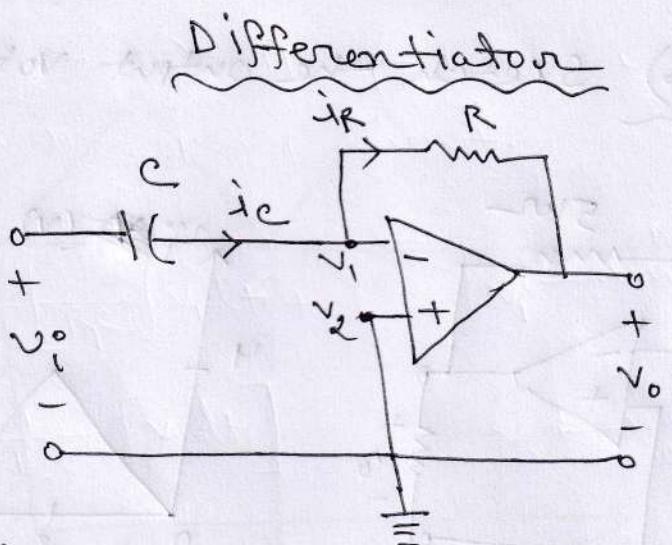

Here,

$$i_C = i_R$$

$$\Rightarrow C \frac{dv_C}{dt} = - \frac{v_1 - v_0}{R}$$



$$\Rightarrow C \frac{d}{dt} (v_i^o - v_1) = - \frac{v_1 - v_0}{R}$$

$$\Rightarrow C \frac{dv_i^o}{dt} = - \frac{v_0}{R} \quad [ \because v_1 = v_2 = 0 ]$$

$$\therefore v_0 = - RC \frac{dv_i^o}{dt}$$

→ X →

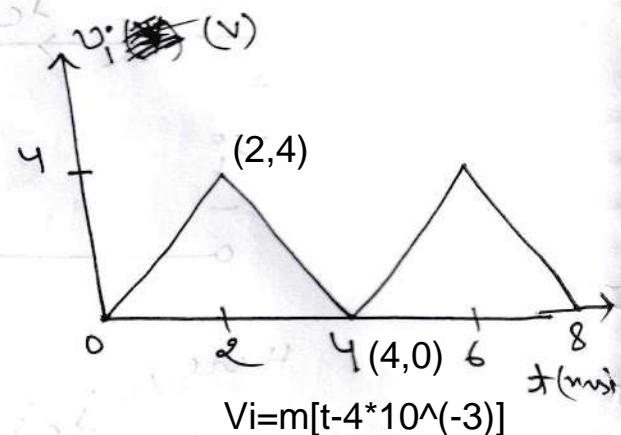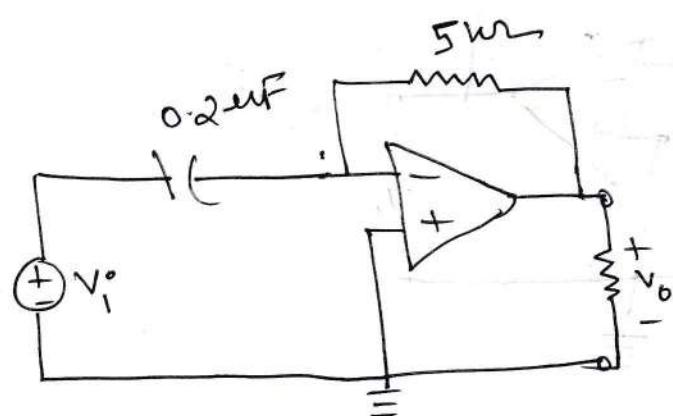Example 6.14 (P-236) Sketch the output voltage for the circuit.



Sol<sup>n</sup>:

Here,

$$RC = 5 \times 10^3 \times 0.2 \times 10^{-6} = 10^{-3} \text{ s}$$

$$v_i = \begin{cases} 2000t, & 0 < t < 2\text{ms} \\ 8 - 2000t, & 2 < t < 4\text{ms} \end{cases}$$

Now, for  $0 < t < 2\text{ms}$ ,

$$v_o = -RC \frac{dv_i}{dt} = -10^{-3} \frac{d}{dt}(2000t) \\ = -2V$$

$$\text{For } 2 < t < 4\text{ms}, \quad v_o = -RC \frac{dv_i}{dt} \cancel{\neq 0}$$

$$= -10^{-3} \frac{d}{dt}(8 - 2000t) \\ = 2V$$


Note: use the concept of CSE 248 to get the signal value.  
For  $0 < t < 2\text{ms}$ ,

$$v_i = \frac{4-0}{(2-0) \times 10^{-3}} t \\ = 2000t$$

For  $2 < t < 4\text{ms}$ .

$$v_i = \frac{0-4}{(4-2) \times 10^{-3}} (t - 4 \times 10^{-3}) \\ = -2000(t - 4 \times 10^{-3})$$

$$= 8 - 2000t$$

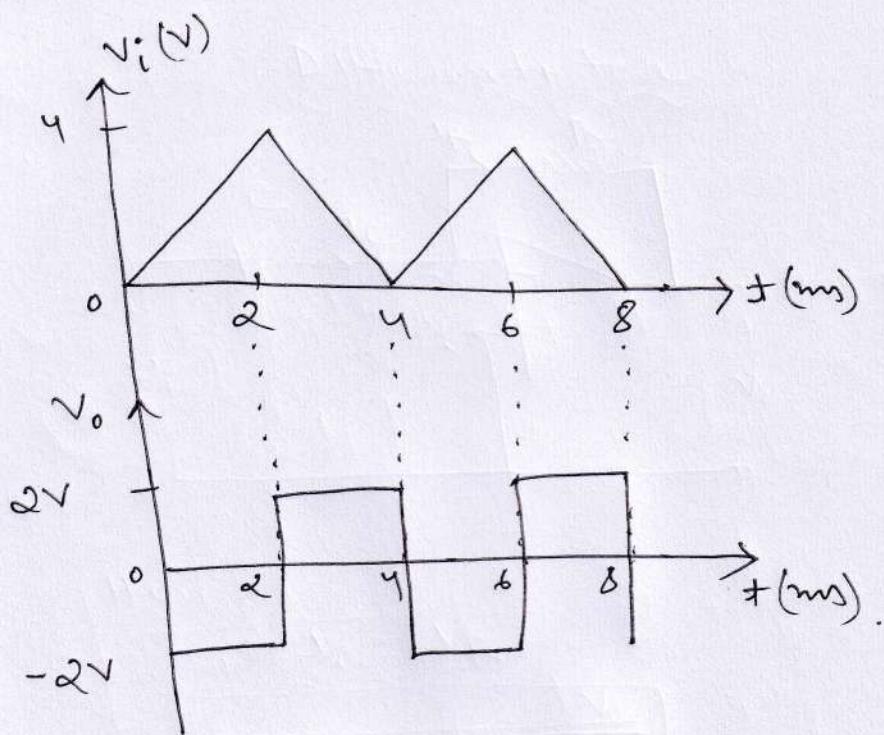


practise: 6.74, 6.75, 6.77 (P-250, 251).

→ X →

Chapter 5  
MOSFET

n-channel MOSFET:

Symbol →

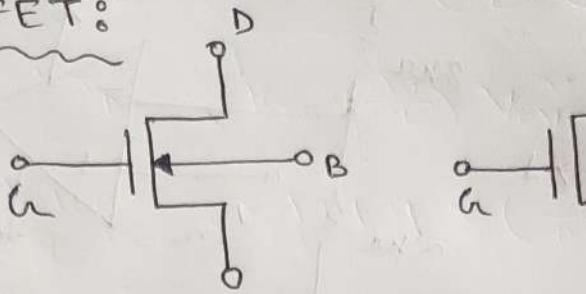

Region of operations of the NMOS transistor

Cut-off	Induced channel	Triode	Saturation
$V_{GS} < V_t$ no channel $i_D = 0$	$V_{GS} \geq V_t$ Overdrive voltage, $V_{OV} = V_{GS} - V_t$	$V_{GS} \geq V_t$ and $V_{DS} > V_t$ $\Rightarrow V_{GS} - V_{DS} > V_t$ $\Rightarrow V_{DS} < V_{GS} - V_t$ $\Rightarrow V_{DS} < V_{OV}$ Drain current, $i_D = \mu_n C_{ox} \left( \frac{W}{L} \right)$ $\left[ (V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$ — (i)	$V_{GS} \geq V_t$ and $V_{DS} \leq V_t$ $\Rightarrow V_{GS} - V_{DS} \leq V_t$ $\Rightarrow V_{DS} \geq V_{GS} - V_t$ $\Rightarrow V_{DS} \geq V_{OV}$ Drain current, $i_D = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)$ $(V_{GS} - V_t)^2$ — (ii)

For small  $V_{DS}$  eqn (ii) becomes,

$$i_D = \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{GS} - V_t) V_{DS}$$

$$\Rightarrow \frac{i_D}{V_{DS}} = \mu_n \left( \frac{W}{L} \right) V_{OV}$$

$$\Rightarrow g_{DS} = \mu_n \left( \frac{W}{L} \right) V_{OV}$$

$$\Rightarrow r_{DS} = \frac{1}{\mu_n \left( \frac{W}{L} \right) V_{OV}}$$

- Example 5.1 Consider a process technology for which  $L_{min} = 0.4 \text{ nm}$ ,  $t_{ox} = 8 \text{ nm}$ ,  $\mu_n = 450 \text{ cm}^2/\text{V.s}$  and  $V_t = 0.7 \text{ V}$ .
- Find  $C_{ox}$  and  $k_m'$ .
  - For a MOSFET with  $W/L = 8 \text{ nm}/0.8 \text{ nm}$ , calculate the values of  $V_{ov}$ ,  $V_{as}$  and  $V_{DSmin}$  needed to operate the transistor in the saturation region with a DC current  $I_D = 100 \text{ mA}$ .
  - For the device in (b), find the values of  $V_{ov}$  and  $V_{as}$  required to cause the device to operate as a  $1000 \Omega$  resistor for very small  $V_{DS}$ .

Sol: (a)  $C_{ox} = \frac{\epsilon_0}{t_{ox}} = \frac{3.9 \epsilon_0}{t_{ox}}$

$$= \frac{3.9 \times 8.854 \times 10^{-12}}{8 \times 10^{-9}} \text{ F/m}^2$$

$$= 4.32 \times 10^{-3} \text{ F/m}^2$$

$= 4.32 \text{ fF/}\mu\text{m}^2$

$$k_m' = \mu_n C_{ox} = 450 \text{ (cm}^2/\text{v.s}) \times 4.32 \times 10^{-3} \text{ (F/m}^2)$$

$$= 450 \times 10^{-4} \times 4.32 \times 10^{-3} \text{ A/V}^2$$

$$= 1.944 \times 10^{-4} \text{ A/V}^2$$

$= 194.4 \text{ }\mu\text{A/V}^2$

(b) For operation in the saturation region,

$$I_D = \frac{1}{2} \mu n C_{ox} \left(\frac{W}{L}\right) (V_{DS} - V_T)^2$$

$$\Rightarrow I_D = \frac{1}{2} k_n' \left(\frac{W}{L}\right) V_{OV}^2$$

$$\Rightarrow 100 = \frac{1}{2} \times 194.4 \times \left(\frac{8}{0.8}\right) \times V_{OV}^2$$

$$\Rightarrow V_{OV} = \boxed{0.321 \text{ V.}}$$

Again,

$$V_{OV} = V_{DS} - V_T$$

$$\Rightarrow V_{DS} = V_{OV} + V_T = 0.321 + 0.7 \\ = \boxed{1.021 \text{ V.}}$$

and  $V_{DS\min} = V_{DS} - V_T = V_{OV} = \boxed{0.321 \text{ V.}}$

(c) we know,

$$r_{DS} = \frac{1}{k_n' \left(\frac{W}{L}\right) V_{OV}}$$

$$\Rightarrow 1000 = \frac{1}{194.4 \times \frac{8}{0.8} \times V_{OV}} \times 10^{-6}$$

$$\Rightarrow \boxed{V_{OV} = 0.52 \text{ V}}$$

Thus,  $V_{DS} = V_{OV} + V_T = 0.52 + 0.7 \\ = \boxed{1.22 \text{ V.}}$

Practise 5.2 (P-261).

Example 5.3: Design the circuit below: that is determine the values of  $R_D$  and  $R_S$  so that the transistor operates at  $I_D = 0.4 \text{ mA}$  and  $V_D = +0.5 \text{ V}$ . The NMOS transistor has  $V_T = 0.7 \text{ V}$ ,  $\mu nCox = 100 \text{ mA/V}^2$ ,  $L = 1 \text{ um}$  and  $W = 32 \text{ um}$ .


Sol:

Here,

$$R_D = \frac{V_{DD} - V_D}{I_D}$$

$$= \frac{2.5 - 0.5}{0.4}$$

$$= 5 \text{ k}\Omega.$$

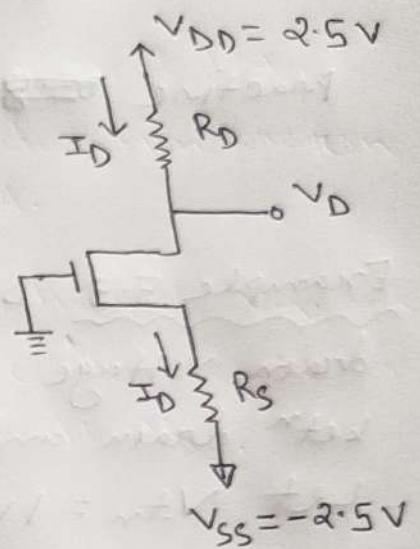

$$\text{Now, } V_{UD} = V_U - V_D$$

$$= 0 - 0.5$$

$$= -0.5 \text{ V}$$

which is less than  $V_T$ . Therefore, the NMOS transistor is operating in the saturation region.

$$\therefore I_D = \frac{1}{2} \mu nCox \left( \frac{W}{L} \right) (V_{US} - V_T)^2$$

$$\Rightarrow 0.4 = \frac{1}{2} \times (100 \times 10^{-3}) \times \left( \frac{32}{1} \right) (V_{US} - 0.7)^2$$

$$\Rightarrow 0.25 = (V_{US} - 0.7)^2$$

$$\Rightarrow V_{US} = 0.5 + 0.7$$

$$\Rightarrow V_U - V_S = 1.2$$

$$\Rightarrow V_S = -1.2 \text{ V.}$$

$$\therefore R_S = \frac{V_S - V_{SS}}{I_D}$$

$$= \frac{-1.2 - (-2.5)}{0.4}$$

$$= 3.25 \text{ k}\Omega.$$

Practise D5.8 (P-278).

D5.9 (P-279)

Example 5.5 Design the circuit to establish a drain voltage of 0.1 V. What is the effective resistance between drain and source at this operating point?

Let  $V_{dm} = 1\text{V}$  and  $k'n(\frac{W}{L}) = 1 \text{ mA/V}^2$ .

Here,

$$V_a = V_{DD} = 5\text{V}$$

$$V_D = 0.1\text{V}, V_S = 0\text{V}$$

$$\therefore V_{US} = V_a - V_S = 5\text{V}$$

$$\therefore V_{UD} = V_a - V_D = 5 - 0.1$$


$$= 4.9\text{V}$$

which is higher than  $V_t$ . Therefore, the NMOS transistor is operating in triode region.

$$\therefore I_D = k'n(\frac{W}{L}) [(V_{UD} - V_t)V_{DS} - \frac{1}{2}V_{DS}^2]$$

$$= 1 \times [5 - 1 \times 0.1 - \frac{1}{2}(0.1)^2]$$


$$= 0.395 \text{ mA.}$$

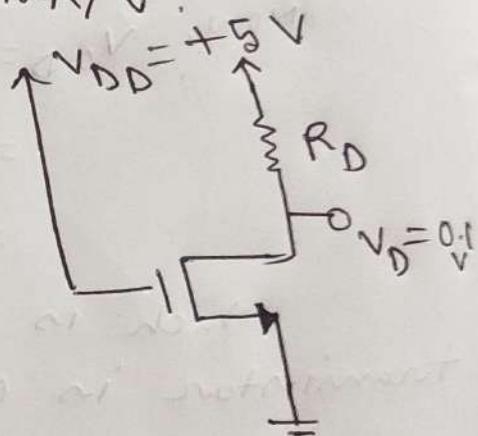

$$\begin{aligned}\therefore R_D &= \frac{V_{DD} - V_D}{I_D} \\ &= \frac{5 - 0.1}{0.395} \\ &= 12.4 \text{ k}\Omega.\end{aligned}$$

The effective drain to source resistance is,
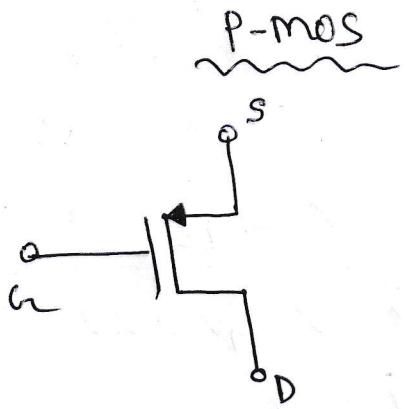
$$r_{DS} = \frac{V_{DS}}{I_{DS}} = \frac{0.1}{0.395} = 253 \Omega.$$



### Region of operation of the PMOS transistor

Cut-off	Induced channel	Triode	Saturation
$V_{SG} <  V_{tp} $ no channel $i_D = 0$	$V_{SG} \geq  V_{tp} $ Overdrive voltage, $ V_{ov}  = V_{SG} -  V_{tp} $	$V_{SG} \geq  V_{tp} $ and $V_{DG} >  V_{tp} $ <del><math>V_{SD} \geq V_{SG} -  V_{tp} </math></del> $\Rightarrow V_{SD} \leq V_{SG} -  V_{tp} $ $\Rightarrow V_{SD} \leq  V_{ov} $ Drain current, $i_D = \mu_p C_{ox} \left( \frac{W}{L} \right)$ $\left[ (V_{SG} -  V_{tp} ) V_{SD} - \frac{1}{2} V_{SD}^2 \right]$	$V_{SG} \geq  V_{tp} $ and $V_{DG} \leq  V_{tp} $ $\Rightarrow V_{SD} \geq V_{SG} -  V_{tp} $ $\Rightarrow V_{SD} \geq  V_{ov} $ Drain current, $i_D = \frac{1}{2} \mu_p C_{ox} \left( \frac{W}{L} \right) (V_{SG} -  V_{tp} )^2$

### Example 5.7 (P-283)

Design the circuit so that the transistor operates in saturation with  $I_D = 0.5 \text{ mA}$  and  $V_D = +3 \text{ V}$ . Let the PMOS transistor have  $V_{tp} = -1 \text{ V}$  and  $k_p' \left( \frac{W}{L} \right) = 1 \text{ mA/V}^2$ . What is the largest value of  $R_D$  can have while maintaining saturation-region operation?

Solution: The drain current at saturation,

$$I_D = \frac{1}{2} k_p' \left( \frac{W}{L} \right) (V_{SD} - |V_{tp}|)^2$$

$$\Rightarrow 0.5 = \frac{1}{2} \times 1 (V_{SD} - 1)^2$$

$$\Rightarrow V_{SD} = 2$$

$$\Rightarrow V_S - V_D = 2$$

$$\Rightarrow 5 - V_D = 2$$

$$\therefore V_D = 3 \text{ V}$$

$$\text{Now, } V_U = \frac{R_{U2}}{R_{U1} + R_{U2}} \times V_{DD}$$

$$\Rightarrow 3 = \frac{R_{U2}}{R_{U1} + R_{U2}} \times 5$$

~~$\Rightarrow 5R_{U1} = 2R_{U2}$~~


$$\Rightarrow 3R_{U1} = 2R_{U2}$$

$$\therefore \frac{R_{U1}}{R_{U2}} = \frac{2}{3}$$

Therefore, a possible selection is  $R_{U1} = 2 \text{ m}\Omega$  and

$$R_{U2} = 3 \text{ m}\Omega.$$
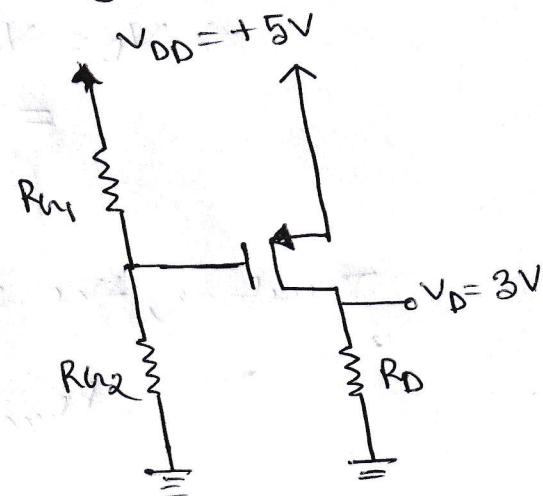
$$\therefore R_D = \frac{V_D}{I_D} = \frac{3}{0.5} = 6 \text{ k}\Omega$$



The minimum condition to maintain saturation mode operation,  $V_{SD} \geq |V_{tp}|$

$$V_{SD} = V_S - V_D - |V_{tp}|$$

$$\Rightarrow V_S - V_D = V_S - V_n - |V_{tp}|$$

$$\Rightarrow V_D = V_n + |V_{tp}|$$

$$= 3 + 1$$

$$= 4 \text{ V}$$

Therefore, the max value of  $R_D$

$$\therefore R_{D\max} = \frac{V_D}{I_D} = \frac{4}{0.5} = 8 \text{ k}\Omega.$$

### Exercise D5.14 (P-285)

Find the value of  $R$  that results in PMOS transistor operating with an overdrive voltage  $|V_{ov}| = 0.6 \text{ V}$ .

The threshold voltage is  $V_{tp} = -0.4 \text{ V}$ ,  $k'_p = 0.1 \text{ mA/V}^2$  and  $W/L = \frac{10 \mu\text{m}}{0.18 \mu\text{m}}$

Solution:

Here,

$$V_{Dn} = V_D - V_n$$

$$= 0 \text{ V}$$

~~$V_{Dn} \geq |V_{tp}| = 0.4 \text{ V}$~~

As  $V_{Dn} \geq |V_{tp}| = 0.4 \text{ V}$ , the PMOS transistor is operating in ~~triode region~~ saturation region

$$\therefore I_D = k'_p \left( \frac{W}{L} \right) \left[ (V_{SD} - |V_{tp}|) \frac{V_{SD}}{2} - \frac{1}{2} \frac{V_{SD}^2}{(1+V_{SD})} \right]$$
 ~~$\Rightarrow 1 \times \frac{10}{0.18} [ (1.8 - 0.4) \frac{1.8}{2} - \frac{1}{2} \frac{(1.8)^2}{(1+1.8)} ]$~~

$$\therefore I_D = \frac{1}{2} k_p' \left( \frac{w}{L} \right) |V_{DS}|^2$$

$$= \frac{1}{2} \times 0.1 \times \left( \frac{10}{0.18} \right) (0.6)^2$$

$$= 1 \text{ mA}$$

$$\therefore R = \frac{1.8 - V_S}{I_D} = \frac{1.8 - 1}{1} = 0.8 \text{ k}\Omega$$

$$= 800 \text{ }\Omega.$$

(Ans.)

$\therefore |V_{DS}| = 0.6$


$\Rightarrow V_{SD} - V_{Dg} = 0.6$

$\Rightarrow V_S - V_A - 0.4 = 0.6$

$\therefore V_S = 1 \text{ V.}$


Practice: 5.49, 5.38, 5.53. [Exercise]
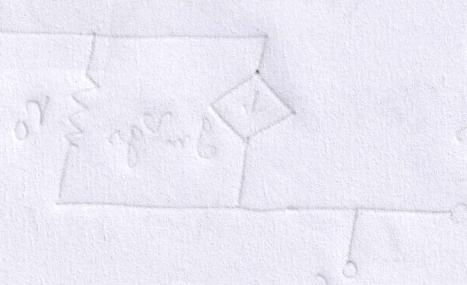
$$I_{DSS} = \frac{A_{DSS}}{R_{DS}} = 0.1 \text{ mA} \quad 200 \text{ mV}$$



Clonatril®  
clonazepam

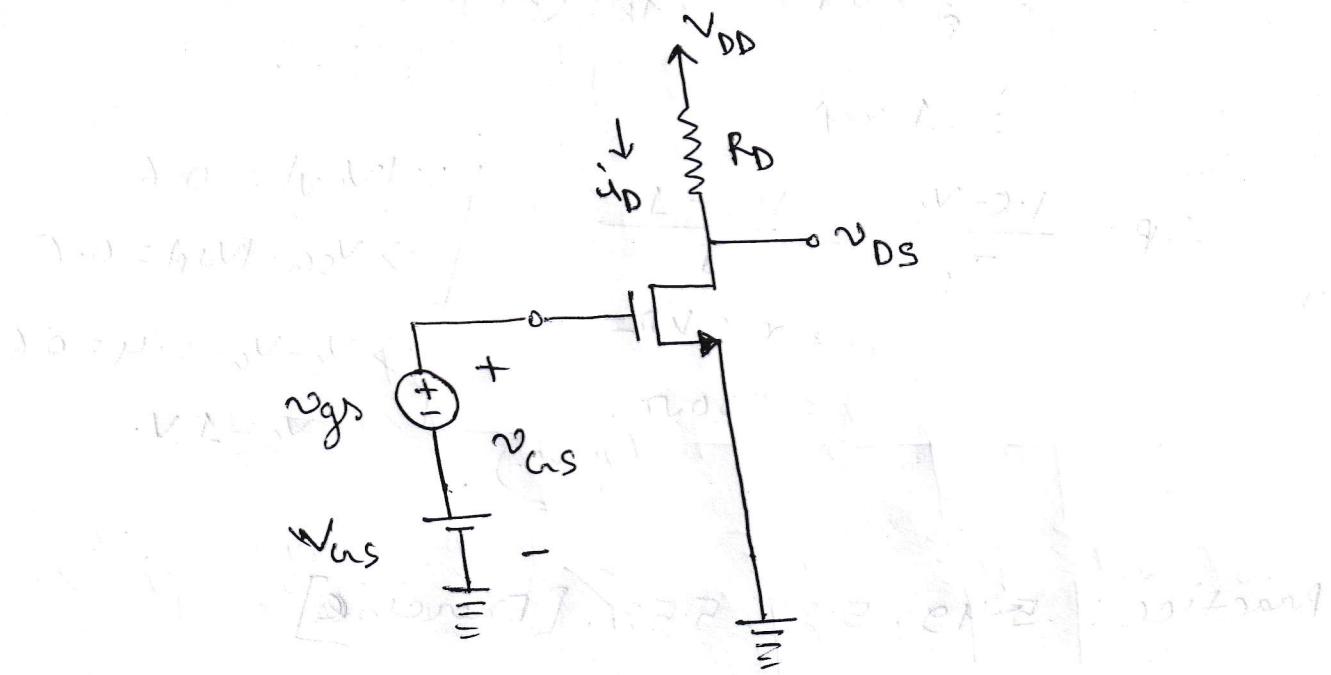\* MOSFET amplifier with a small time-varying signal  $v_{gs}(t)$  superimposed on the dc bias voltage  $V_{GS}$ .



Small-signal condition is,


$$v_{gs} \ll 2(V_{GS} - V_t)$$

$$\text{or } v_{gs} \ll 2V_{ov}.$$

MOSFET transconductance  $g_m \equiv \frac{i_d}{v_{gs}} = \cancel{k_n(\frac{W}{L})(V_{GS}-V_t)} = k_n'(\frac{W}{L})(V_{GS}-V_t)$

Voltage gain,  $A_v \equiv \frac{v_{ds}}{v_{gs}} = -g_m R_D$ .

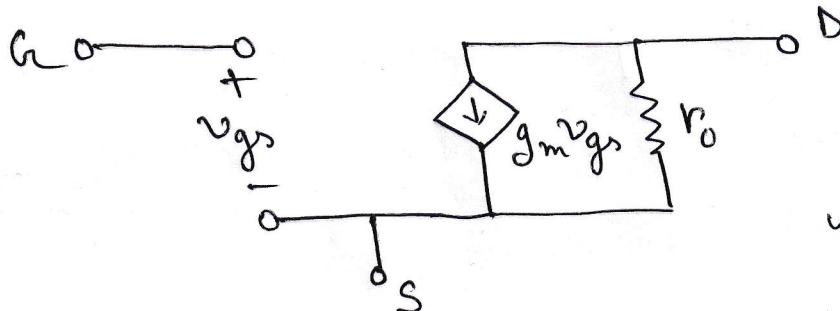Small-signal model including the effect of channel-length modulation



Here,


$$R_o = \frac{1}{\lambda I_D}$$

$$= \frac{V_A}{I_D}$$

where,  
 $V_A = \frac{1}{\lambda}$ .
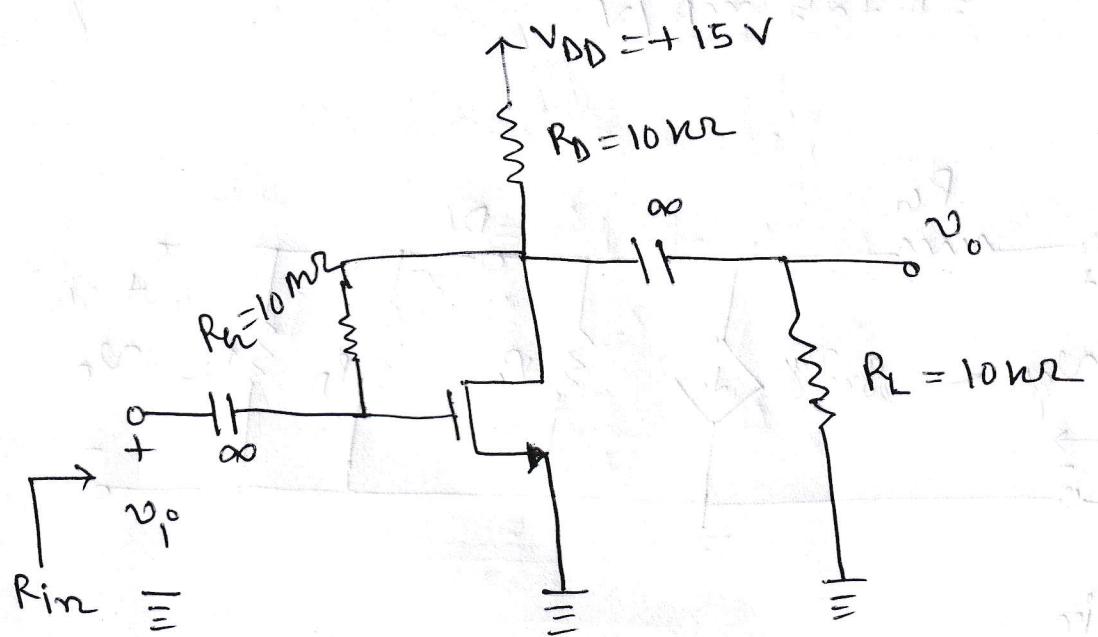
### Example 7.3 (Page 389)

Analyze this amplifier circuit to determine its small signal voltage gain, its input resistance, and the largest allowable input signal. The transistor has  $V_t = 1.5 \text{ V}$ ,  $k_n' \left( \frac{W}{L} \right) = 0.25 \text{ mA/V}^2$ , and  $V_A = 50\text{V}$ .



Sopm  
Ans

As  $I_h = 0$ , here,

$$V_{GS} = 0$$


$$\therefore V_{DS} = V_{DS} = V_{DD} - I_D R_D \\ = 15 - 10 I_D$$

NMOS transistor will be operating in the saturation. Thus,

$$I_D = \frac{1}{2} k_n' \left( \frac{W}{L} \right) (V_{DS} - V_t)^2$$

$$\Rightarrow 2 I_D = 0.25 (15 - 10 I_D - 1.5)^2$$

$$\Rightarrow I_D = 1.06 \text{ mA.}$$

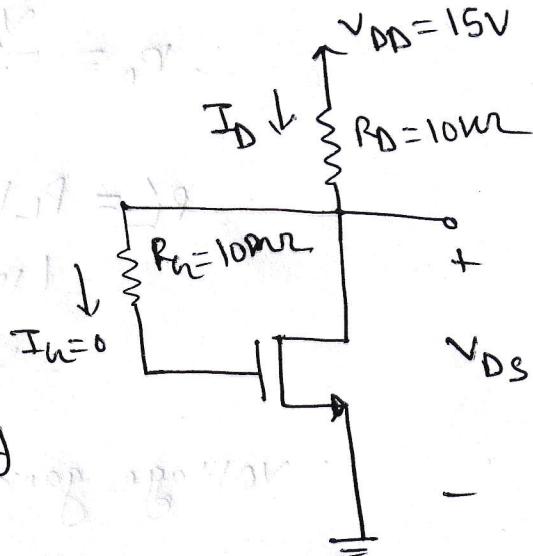

Circuit for determining dc operating point.


**Clonatri®**  
clonazepam

$$\therefore V_{GS} = 15 - (10 \times 1.06) = 4.4 \text{ V.}$$

$$\therefore g_m = k_n' \left( \frac{w}{l} \right) (V_{GS} - V_T)$$

$$= 0.25 \times (4.4 - 1.5)$$

$$= 0.725 \text{ mA/V}$$

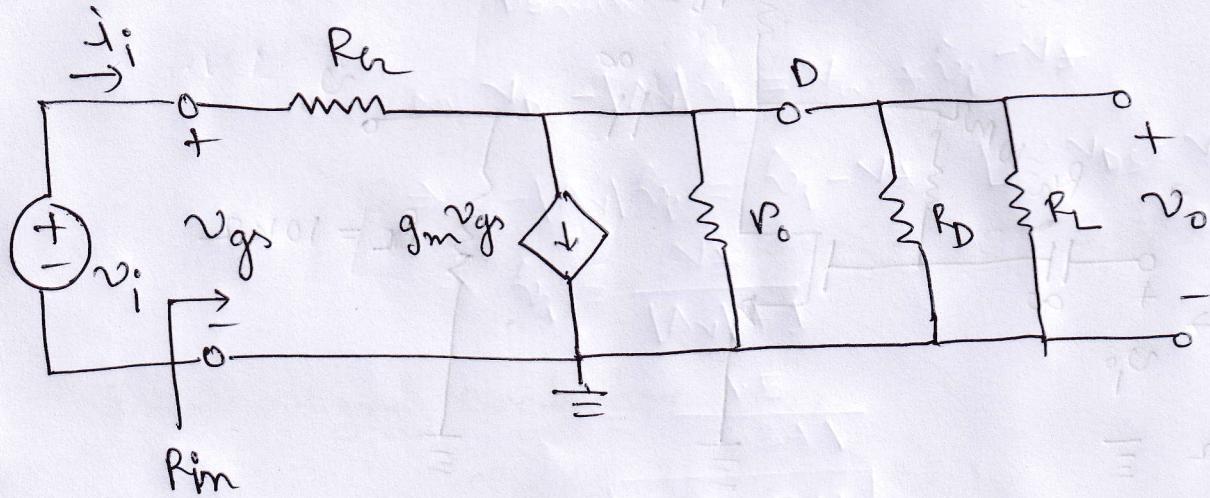

$$\therefore R_o = \frac{V_A}{I_D} = \frac{50}{1.06} = 47 \text{ k}\Omega$$

$$\therefore R'_L = R_L || R_D || R_o$$

$$= (10 || 10 || 4.7) \text{ k}\Omega$$

$$= 4.52 \text{ k}\Omega$$

$$\therefore \text{Voltage gain, } A_v \approx -g_m R'_L$$

$$= -0.725 \times 4.52$$

$$= -3.3$$

We know,

$$Av = \frac{v_o}{v_{gs}}$$

$$\Rightarrow v_o = Av v_{gs}$$

$$\Rightarrow v_o = -g_m R_L v_{gs}$$

$$\therefore R_{in} = \frac{v_i}{i_i} = \frac{v_{gs}}{i_i}$$

$$\Rightarrow R_{in} = \frac{\frac{v_{gs}}{v_i - v_o}}{R_L}$$

$$\Rightarrow R_{in} = \frac{v_{gs} \times R_L}{v_{gs} - v_o}$$

$$= \frac{v_{gs} R_L}{v_{gs} + g_m R_L v_{gs}}$$

$$= \frac{R_L}{1 + g_m R_L}$$

$$= \frac{10 \times 10^3}{1 + 3 \cdot 3}$$

$$= 2.33 \times 10^3 \text{ k}\Omega$$

$$= 2.33 \text{ M}\Omega$$

The largest allowable input signal  $\hat{v}_i$  is constrained by the need to keep the transistor in saturation at all times; that is,

$$V_{DS} \geq V_{GS} - V_T$$

Enforcing the condition with equality,

$$V_{DS\min} = V_{GS\max} - V_T$$

$$\text{or } V_{DS} - |Av| \hat{v}_i = V_{GS} + \hat{v}_o - V_T$$

$$\Rightarrow -|Av| \hat{v}_o = \hat{v}_i - V_T \quad [\because V_{DS} = V_{GS}]$$

$$\Rightarrow \hat{v}_i = \frac{V_T}{|Av| + 1}$$

$$= \frac{1.5}{3.3 + 1}$$

$$= 0.35 \text{ V}$$

practice:

7.29, 7.31, 7.32 (P-485).

